

Load test on Single phase induction Transformer

AIM:

Load test on a single phase transformer is conducted to evaluate the transformer's performance under full load condition.


Apparatus Required:

S.No	Apparatus	Range	Quantity.
1	Single phase transformer	1 Φ (0 - 260V)	1
2.	Voltmeter	(0 - 150), (0, 300) M1-type	1 each
3.	Ammeter	(0 - 10)V (0 - 5V) M1-TYPE	3 each
4.	Wattmeter	300V, SA 150V, SA; UPF	1 each
5.	AC Power Source		
6	Variable resistive load	5kA, 250V	1
7.	Connecting wires	-	As required.

PROCEDURE:

- Connect the circuit as per required
- Supply the rated voltage to primary winding using auto transformer.

Circuit Diagram:

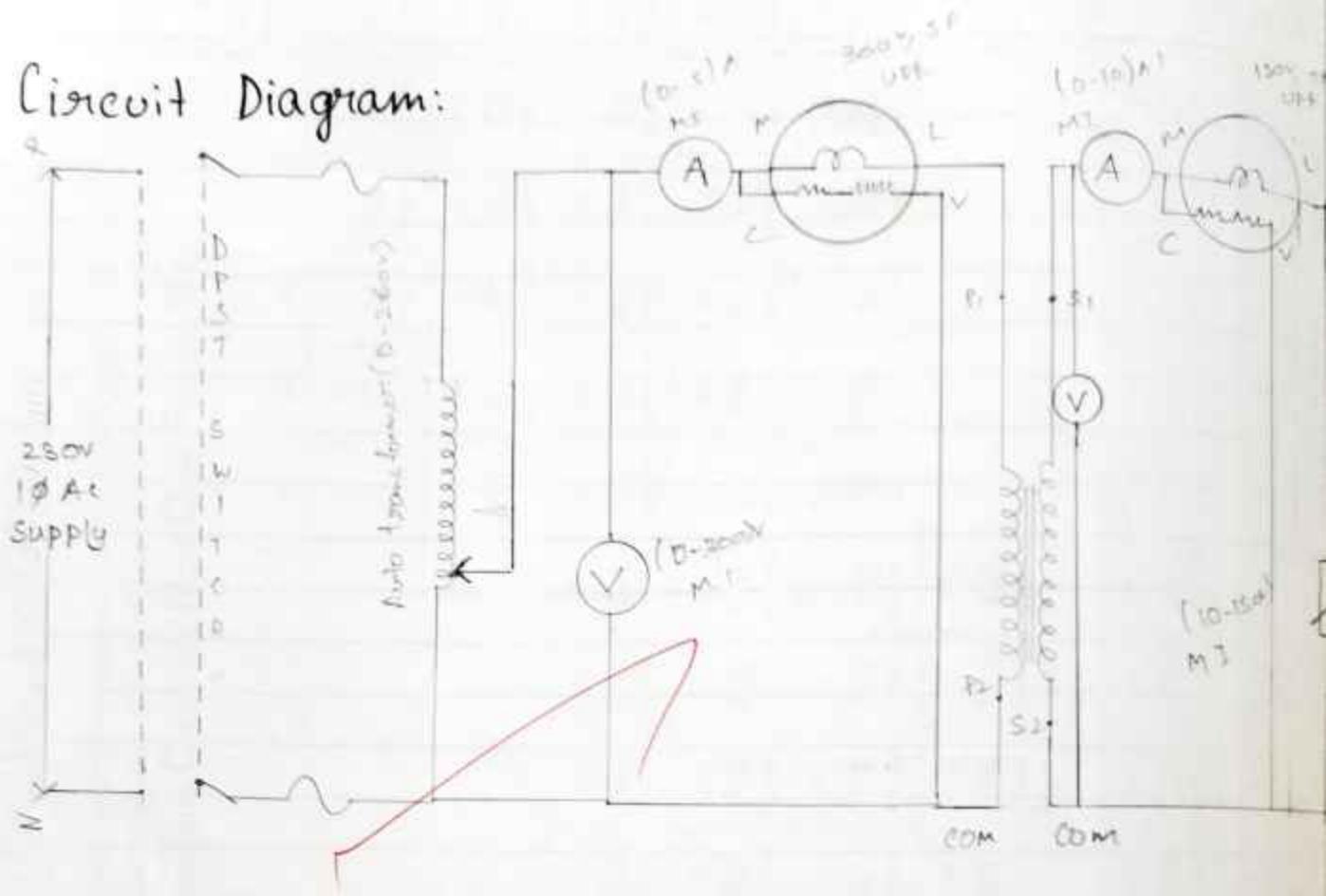

TABULATION:

MF = 2

S.No.	Load current (I_2)	Secondary voltage (v_2)	Primary current (i_1)	Primary voltage (v_1)	W. Power + W ₂			Efficiency (%)	Voltage regulation
					0.00	110	0.00		
1	0.2 A	220	0.21	220	60	120	0	0	0%
2	0.4 A	218	0.42	220	108	216	18	36	16.67%
3	0.6 A	216	0.63	220	128	250	30	120	48%
4	0.8 A	214	0.84	220	160	320	55	230	68.75%
5	1.0 A	212	1.05	220	210	420	86	344	81.90%

- Adjust the Load
- Note the readings of primary voltage(V_1), Primary current(I_1), secondary voltage(V_2), Secondary current(I_2), power consumed by the load (P)
- Calculate the voltage regulation $\% = \frac{V_2 - V_1}{V_1} \times 100$
- Calculate the efficiency (n) = $\frac{\text{Output}}{\text{Input}} \times 100$
- Analyse the results.

~~Ques~~

~~RESULTS:~~ Thus the load test on single phase transformer is conducted.

Efficiency:

$$\text{Voltage}(\%) = \frac{V_1 - V_2}{V_2} \times 100$$

$$\eta = \frac{\text{Output}}{\text{Input}} \times 100$$

$$1) \eta = \frac{220 - 212}{220} \times 100 = 8\%$$

$$\eta = \frac{P_o}{P_i} \times 100 = \text{?}%$$

$$2) \frac{220 - 212}{212} \times 100 = 0.92\%$$

$$\eta = \frac{24}{216} \times 100 = 16.67\%$$

$$3) \frac{220 - 216}{216} \times 100 = 1.85\%$$

$$\eta = \frac{110}{250} \times 100 = 42\%$$

$$4) \frac{220 - 214}{214} \times 100 = 2.81\%$$


$$\eta = \frac{220}{310} \times 100 = 68.75\%$$

$$5) \frac{220 - 212}{212} \times 100 = 3.78\%$$

$$\frac{344}{450} \times 100 = 76.44\%$$

Load Test on Single Phase Transformer

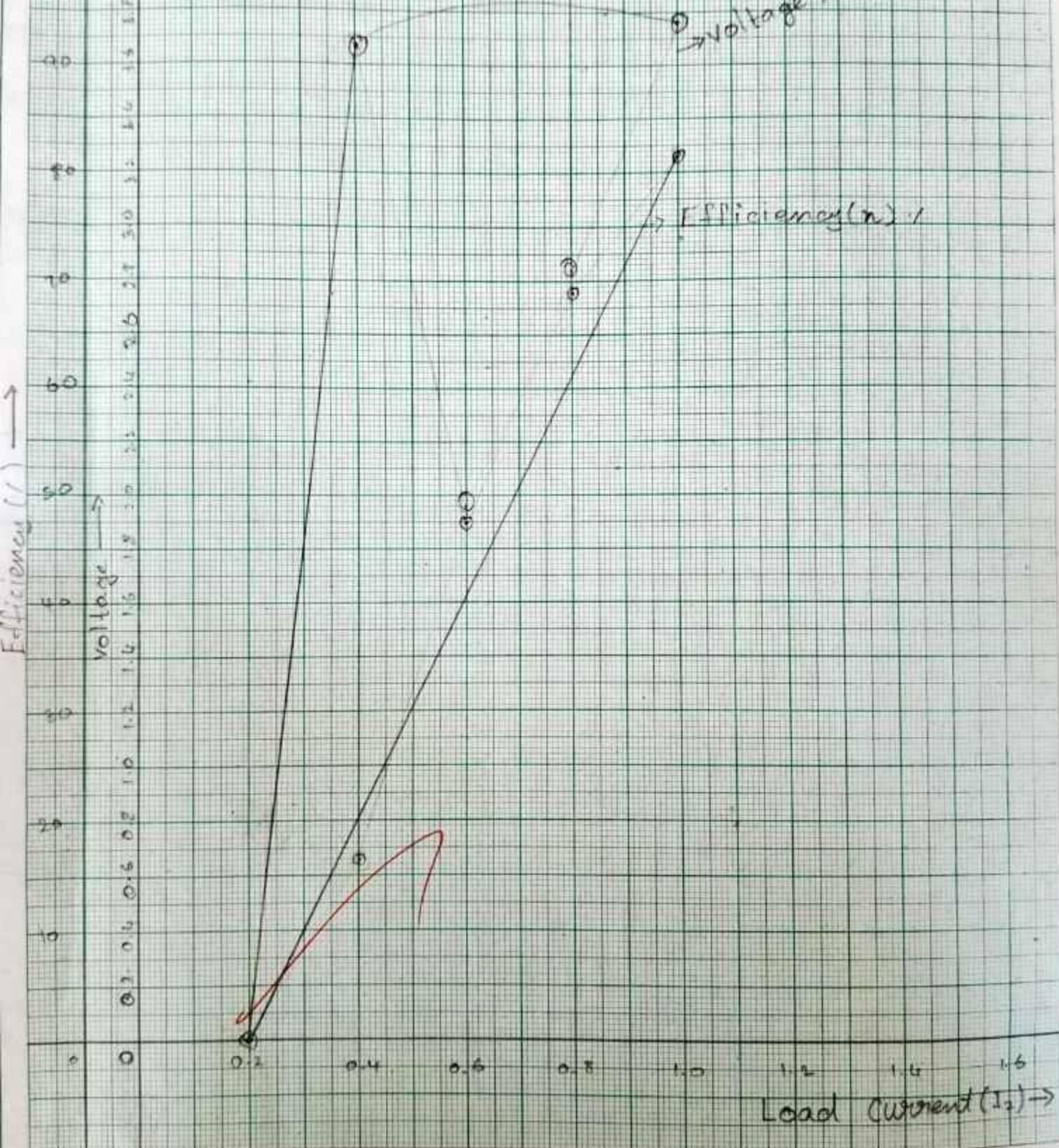Scale
 Variation = 1 unit
 Gain 100 - 1000



OC & SC test on Single Phase transformer.

AIM: To conduct load test on single phase transformer E_2 to find efficiency & percentage regulation.


APPARATUS REQUIRED:

S.NO	APPARATUS	RANGE	TYPE	QUANTITY
1	Ammeter	(0-10)A (0-5)A	M1 M1	1 1
2	Voltmeter	(0-150)V (0-300)V	M1 M1	1 1
3	Wattmeter	(300V, 5A) (150V, 5A)	UPF UPF	1 1
4	Auto transformer.	1Φ, (0-250)V	-	1
5	Resistive Load	5KW, 230V	-	1
6	Connecting wires.	2.5 Sq mm	Copper	few


PROCEDURE:

- Connect the Primary winding to a variable AC Supply.
- Run the transformer with no load connected. Measure the Load secondary voltage.
- Gradually Increase the Load on the secondary

Circuit Diagram:

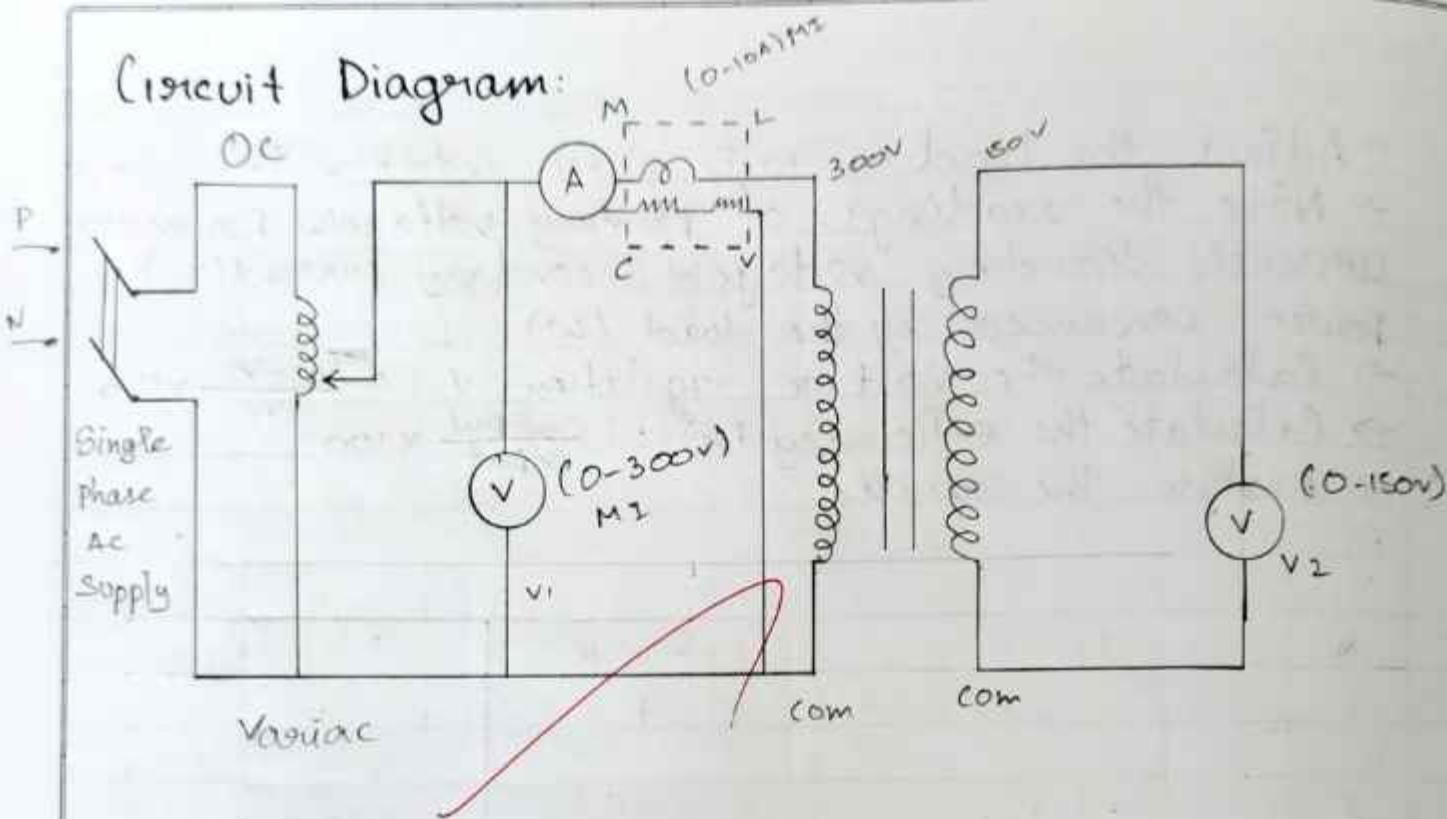

SC

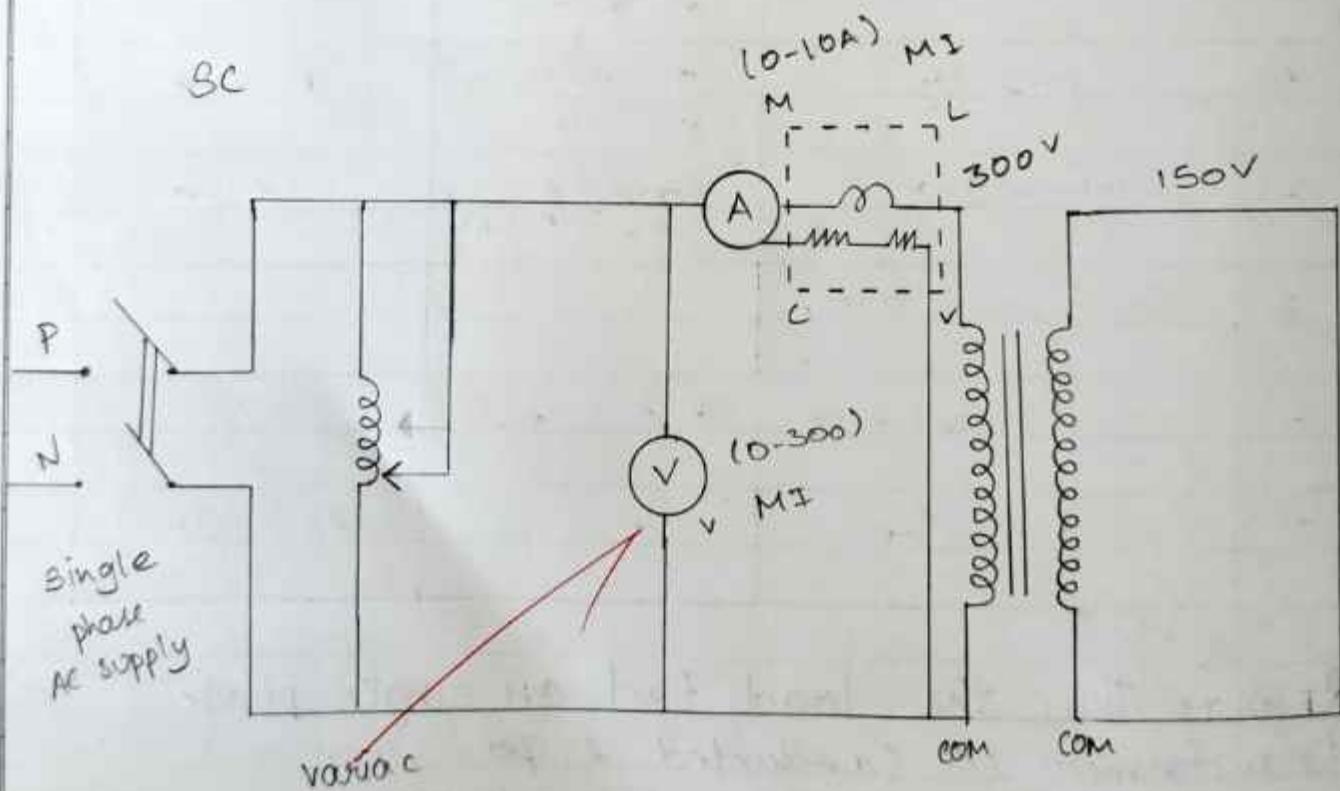

- Calculate the voltage Regulation = $\frac{V_2 - V_1}{V_1} \times 100$
- Calculate efficiency $O.P/I.P \times 100$.
- Analyse the results.

(10)

(2) of 12

~~RESULT: Thus the OC & SC test on single phase transformer is conducted.~~

OC Test

$$MF = 4$$

V_1	I_1	W_1	V_2
220 V	0.5 A	OBS 5 ACT 10	110 V

SC Test

$$MF = 4$$

V_1	I_1	W_1	I_2
115	2 A	OBS 3 ACT 12	4 A


Calculation of Secondary turns and current in a transformer.

AIM: To evaluate secondary turns & current in an transformer & to find voltage regulation efficiency & overall behaviour of transformer when it is delivering power to load.

APPARATUS REQUIRED:

S.NO	APPARATUS	RANGE	QUANTITY
1.	Single - phase transform	1Φ, (0-260)v	1
2.	Voltmeter	(0-150v), (0-300v)v, MI	1 Each
3.	Ammeter	(0-10A); (0-5) A MI	1 Each
4.	Wattmeter	(300v, 5A) (150v, 5A)	1 Each
5.	AC Power Supply		
6.	Variable resistive load	5KW, 230V	1
7.	Connecting wires	As required	

Circuit

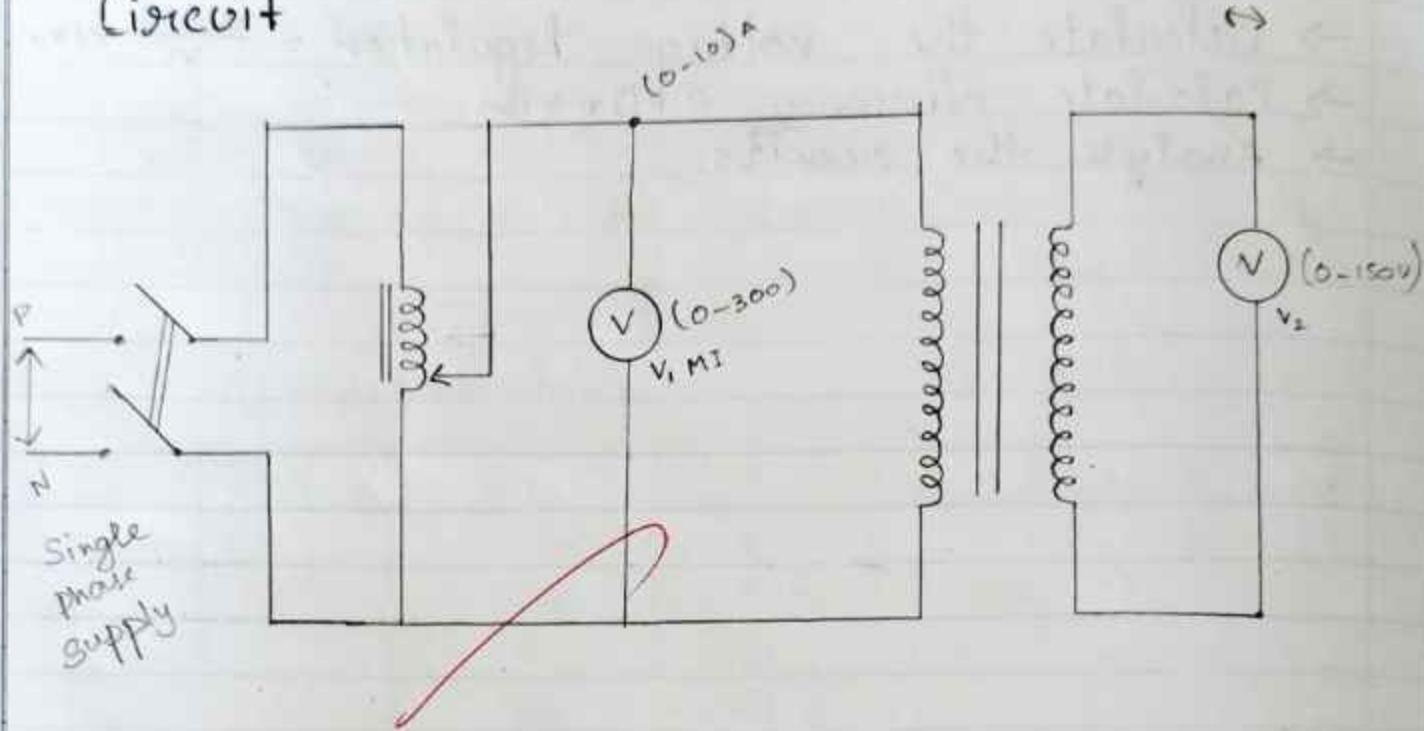

$$\frac{V_2}{V_1} = K = \frac{N_2}{N_1} = N_2 = N_1 \times K$$

$$N_2 = 110$$

$$N_2 = \frac{1}{2} \times 110$$

$$N_2 = 55.$$

SO	V_1	V_2	K	N_1	N_2
1	60	30	$\frac{1}{2}$	110	55
2	80	40	$\frac{1}{2}$	110	55
3	120	60	$\frac{1}{2}$	110	55
4	740	70	$\frac{1}{2}$	110	55
5	160	80	$\frac{1}{2}$	110	55

PROCEDURE:

- A transformer operates on the principle of electromagnetic induction & consists of primary winding & secondary winding.
- Before performing calculations, gather - the required parameters like V_p , N_p , I_p , V_s .
- Calculate Secondary turns (N_s) = $(V_s/V_p) \times N_p$
- Calculate Secondary current (I_s) = $(N_p/N_s) \times I_p$
- Analyse the result.

~~P~~
~~Q~~ ~~S~~ ~~T~~

RESULT: By following, we can calculate the turns and current in a Transformer. This can be adopted for any set of input values.

Calculations:

$$\frac{V_2}{V_1} = K = \frac{N_2}{N_1}$$

$$N_2 = N_1 \times K$$

$$N_1 = 110$$

$$N_2 = \frac{1}{2} \times 110$$

$$N_2 = 55$$

Load test on Single phase induction motor

AIM: To conduct load test on the given single phase induction motor & to plot its performance characteristics, (ie) electrical characteristics - speed, torque, slip, power factor & efficiency vis output power.



APPARATUS REQUIRED:

S.NO	APPARATUS	SPECIFICATIONS	QUANTITY
1.	Voltmeter	(0-300V) MI	1
2.	Ammeter	(0-10A) MI	1
3.	wattmeter	(300V, 10A) UPF	1
4.	Tachometer	(0-10000)RPM	1

PROCEDURE:

- Connections as per circuit diagram.
- The ~~DPST~~ Switch is closed & single phase Supply is given
- Adjust the variac to apply the voltage
- The procedure is repeated till rated current of the machine

Circuit Diagram:

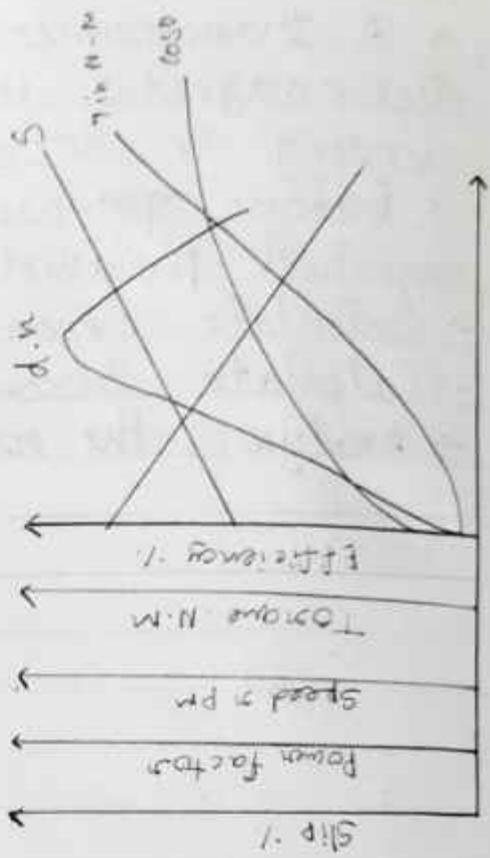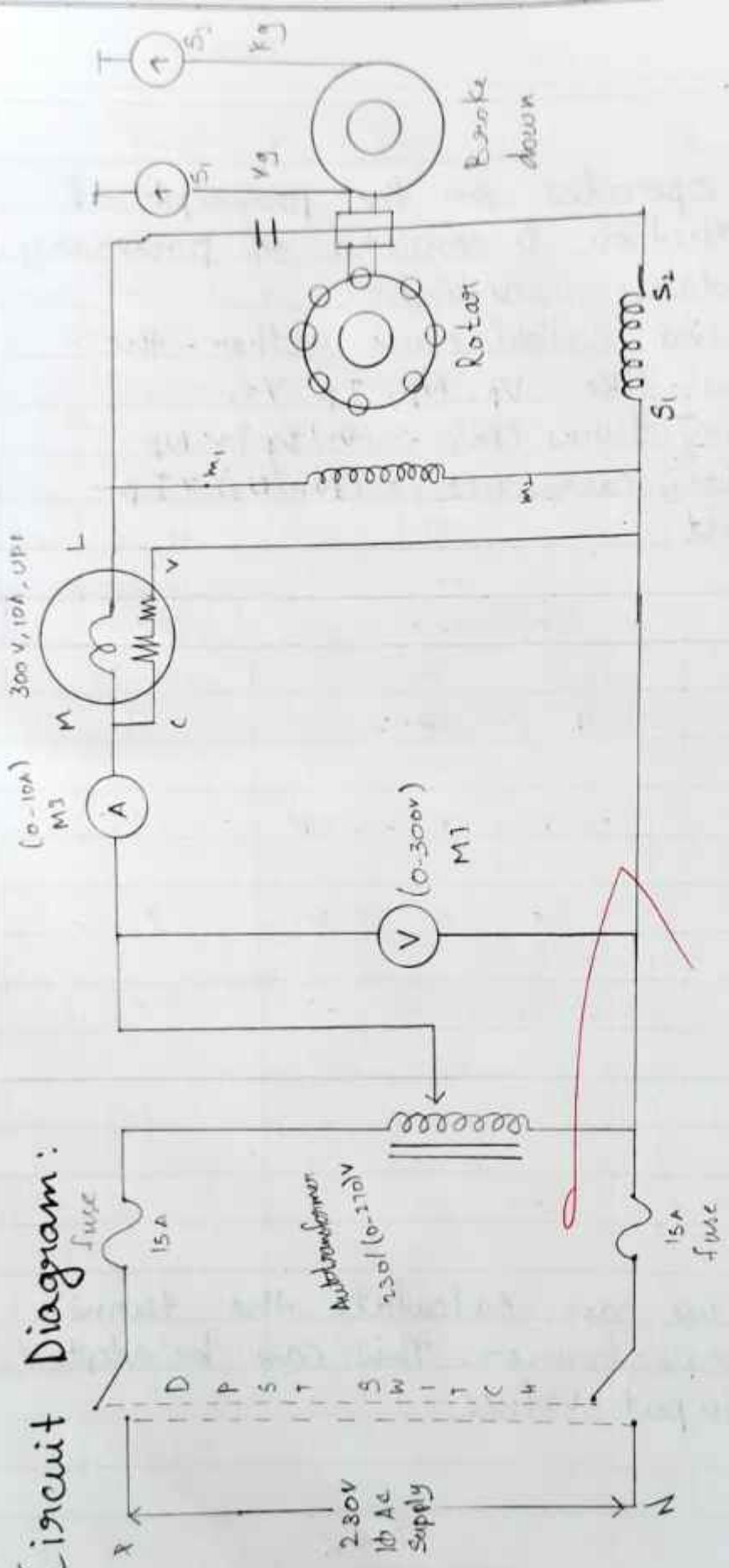

- The motor is unloaded, the auto-transformer is brought to the min voltage.
- The radius of the brake drum is measured.

Formula:

- Circumference of ~~brake drum~~ = $2\pi R$
- Input power watts (ω)
- Torque = $9.8 \times R \times (S_1 - S_2)$ (N-m)
- Output power = $\frac{2\pi NT}{60}$ (watts)
- $(n) = \frac{O.P / T.P \times 100}{60}$
- $WS\phi = \omega / VT$
- $S = \frac{N_s - N}{N_s} \times 100$

09
10
~~SI~~

~~RESULT~~: Thus the load test was conducted on 1Φ induction motor & its performance characteristics were down.

MF = 8

Speed (rps)	Torque Nm	Current Amps	Wattmeter		Efficiency		Torque 1/3 full load Nm	O/P W Watt	Eff. %
			DC	AC	Eff.	Power			
220	2.0	1425	60	240	0	0	0	0	0
220	3.0	1420	105	420	3	1	2.35	349.27	0.636
220	3.5	1415	150	500	6	2	4.70	696.08	0.779
220	4.0	1410	190	760	9	4	5.88	861.61	0.863
220	4.5	1400	220	880	10	5	5.88	861.61	0.863

Solutions:

Torque : $T = 9.81 \times R \times (s_1 - s_2)$

$$9.81 \times 0.12 \times 0 = 0$$

$$9.81 \times 0.12 \times 2 = 2.35$$

$$9.81 \times 0.12 \times 4 = 4.70$$

$$9.81 \times 0.12 \times 5 = 5.88$$

$$9.81 \times 0.12 \times 5 = 5.88$$

Output power = $27 \text{ NT} / 60$

$$1) 2 \times 3.14 \times 1425 \times 0 / 60 = 0$$

$$2) 2 \times 3.14 \times 1420 \times 2.35 / 60 = 349.27$$

$$3) 2 \times 3.14 \times 1415 \times 4.70 / 60 = 696.08$$

$$4) 2 \times 3.14 \times 1410 \times 5.88 / 60 = 861.61$$

$$5) 2 \times 3.14 \times 1400 \times 5.88 / 60 = 861.61$$

over Output = $O/I = 0.636$

$$420 / 220 \times 0.636 = 0.636$$

$$620 / 220 \times 0.636 = 0.636$$

$$600 / 220 \times 3.5 = 0.779$$

$$760 / 220 \times 4.0 = 0.863$$

$$780 / 220 \times 4.5 = 0.863$$

Efficiency $\eta = O/I P$

$$1) 0 / 220 \times 3.0 = 0 \times 100 = 0$$

~~$$2) 349.27 / 220 \times 3.0 = 0.529 \times 100 = 52.9$$~~

~~$$3) 696.08 / 220 \times 3.5 = 0.904 \times 100 = 90.4$$~~

~~$$4) 861.61 / 220 \times 4.0 = 0.979 \times 100 = 97.9$$~~

~~$$5) 861.61 / 220 \times 4.5 = 0.870 \times 100 = 87.0$$~~

Slip : $\frac{N_s - N_m}{N_s} \times 100$


$$1) \frac{1500 - 1425}{1500} \times 100 = 0.05 \times 100 = 5\%$$

$$2) \frac{1500 - 1420}{1500} \times 100 = 0.053 \times 100 = 5.3\%$$

$$3) \frac{1500 - 1415}{1500} \times 100 = 5.66\%$$

$$4) \frac{1500 - 1410}{1500} \times 100 = 6.67\%$$
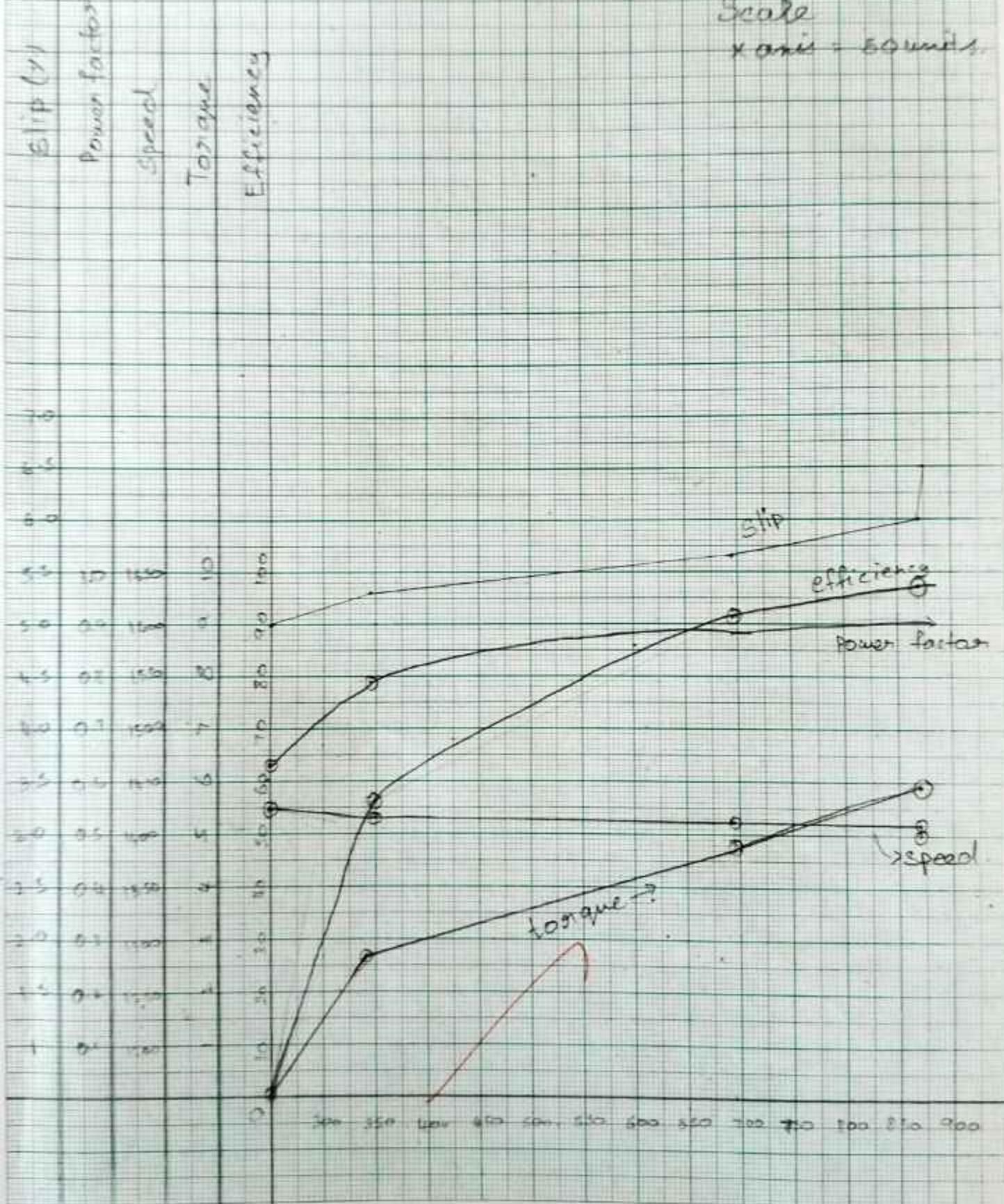
$$5) \frac{1500 - 1400}{1500} \times 100 = 6.67\%$$



Measurement of power by two wattmeters Method.


AIM: 3 phase, three wire power measurement by using 2 wattmeter method for a balanced load in star connection.

PROCEDURE:

- Watt meter UPF 600V, $\frac{1}{2}$ Amps - 2 Nos
- Balanced resistive load 3phase, 3A - 10Wos
- 3 phase variac 415 V/470, 4A, 1NO's.
- Digital AC Voltmeters 600V - 1no.
- Connect the load with help of switches & patch chords
- Connect the 3 phase variac to the main supply
- Connect the voltmeter across 2 phases.
- Connect the circuit as shown below either in star connection.

~~RESULT: Hence, the power measured for a balanced load connected in star is the sum of both Watt meter.~~

Circuit Diagram:

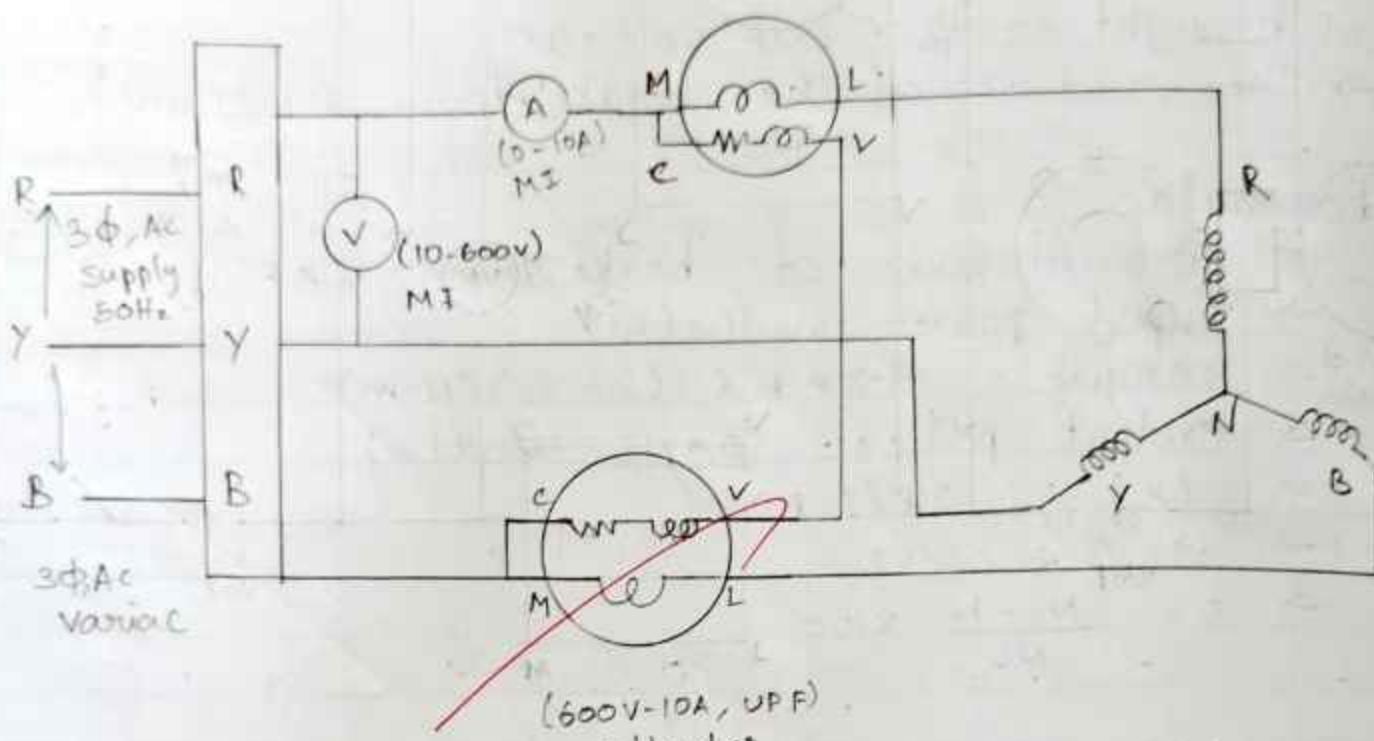

$$\cos\phi = \frac{P}{V_L \times I_L}$$

MF = 8

S.No	V _L	I _L	W ₁		W ₂		P: W ₁₊₂	$\cos\phi^1$	$P_{\text{ref}} \frac{\sqrt{3}V_L}{2}$
			Obs	Act+	Obs	Act+			
1	415	2.5	110	880	0	0	880	0.84	871.5
2	415	3.0	155	1240	45	360	1600	1.28	1594
3	415	2.5	160	1280	50	400	1680	1.15	1670.37

$$1) \frac{880}{415 \times 2.5} = 0.84$$

$$3) \frac{1680}{415 \times 2.5} = 1.15$$

$$1) 415 \times 2.5 \times 1 \times 0.84 = 871.5$$

$$2) 415 \times 3.0 \times 1 \times 1.28 = 1594$$

$$3) 415 \times 3.5 \times 1 \times 1.15 = 1670.37$$


$$2) \frac{1600}{415 \times 3.0} = 1.28$$

Calculate the energy consumption using the energy meter.

AIM: To calibrate & test the given single phase energy meter by direct loading.

APPARATUS REQUIRED:

S.No	Apparatus	Type	Range	Quantity.
1.	Single phase energymeter	Induction	1500REV/kWh	1
2.	Wattmeter	UPR	300V/15A	1
3.	Voltmeter	MI	(0-300)V	1
4.	Ammeter	MI	(0-5)A	1
5.	Single phase Variac	1-Φ v, 10A	230V/(0-270)	1
6.	Rheostat	WW	110Ω/15A	1
7.	Stopwatch	digital	-	1
8.	Connecting wires.	-	-	required.

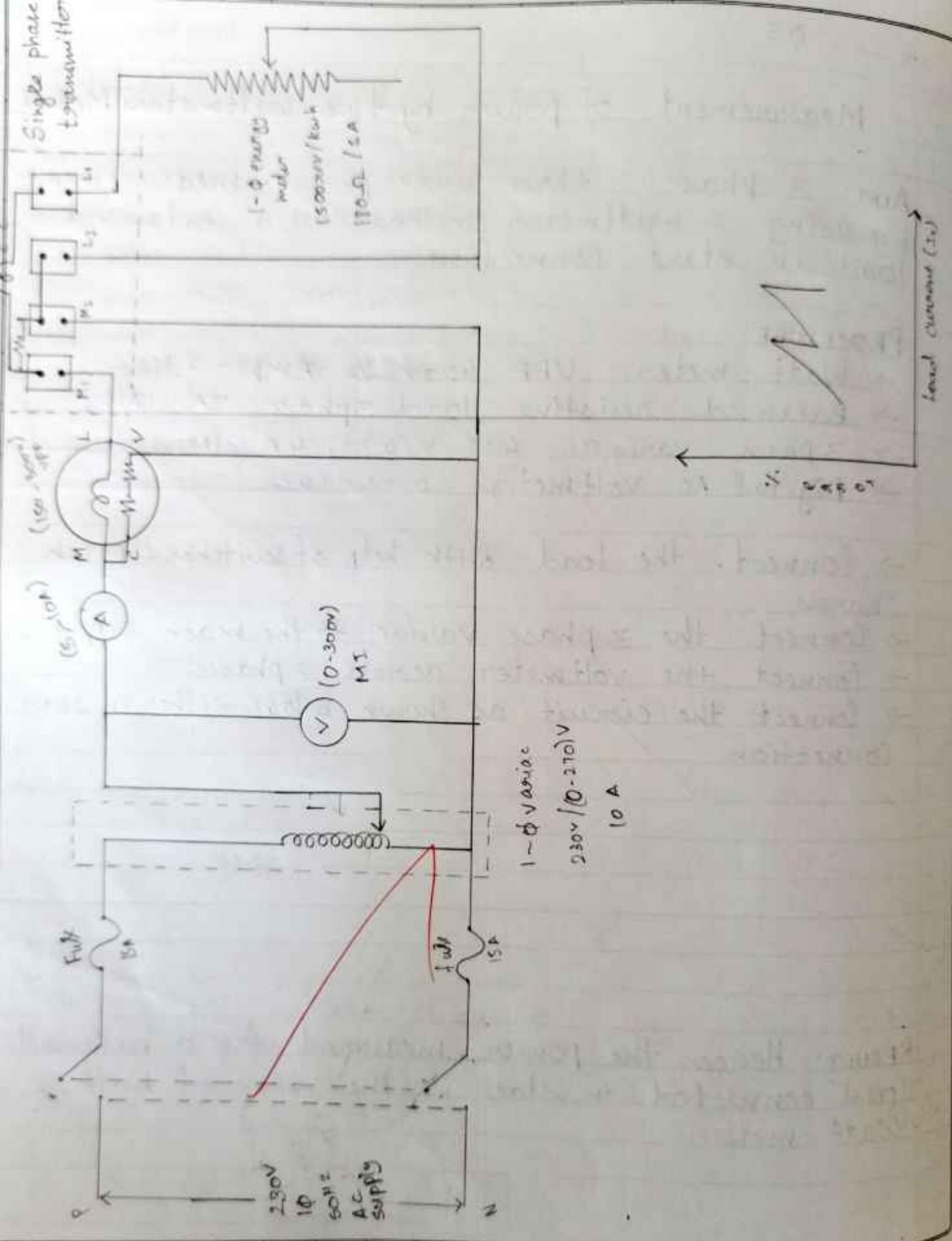

PROCEDURE :

- Connect the circuit as per circuit diagram
- keep the single phase variac at zero volt position
- Now switch on the power supply.
- Gradually vary the variac to apply the rated voltage (230v)
- For diff values of load, notedown the readings of the ammeter, voltmeter & time taken for 10 resolution
- Gradually vary the variac, 10 minimum or zero volt position.
- Switch off the supply.
- Calculate Observed reading, actual reading.
- Draw the Graph.

(10)
10
~~Set 12~~

~~RESULT: Hence the calibrate & test the single phase energy meter by direct loading is done.~~

TABULATION:

No.	Velocity (m)	Amplitude (A)	Wavelength (m)	Time for 1 sec	Theoretical Period (T)	Practical Period (T)	Error %
1	230	0.5	20	41.63	13.87	0.231	- 98%
2	230	1	40	38.38	12.79	0.426	- 90%
3	220	2.0	65	25.60	8.53	0.462	- 98%
4	220	2.5	70	24.07	8.02	0.468	- 94%
5	220	3.0	85	17.64	5.88	0.416	- 85%

CALCULATION:

Theoretical Reading

$$1) E_1 = \frac{1200}{3600} \times 41.63 = 13.87$$

$$2) E_2 = \frac{1200}{3600} \times 38.38 = 12.79$$

$$3) E_1 = \frac{1200}{3600} \times 25.60 = 8.53$$

$$4) E_2 = \frac{1200}{3600} \times 24.07 = 8.02$$

$$5) E_1 = \frac{1200}{3600} \times 17.64 = 5.88$$

Practical Reading

$$E_2 = \frac{2.0 \times 41.63}{3600} = 0.231$$

$$E_2 = \frac{4.0 \times 38.38}{3600} = 0.426$$

$$E_2 = \frac{6.5 \times 25.60}{3600} = 0.462$$

$$E_2 = \frac{7.0 \times 24.07}{3600} = 0.468$$

$$E_2 = \frac{8.5 \times 17.64}{3600} = 0.4165$$

Errors (%)

$$1) \frac{0.231 - 13.87}{13.87} \times 100 = -98\%$$

$$4) \frac{0.468 - 8.02}{8.02} \times 100 = -94\%$$

$$2) \frac{0.426 - 12.79}{12.79} \times 100 = -90\%$$

$$5) \frac{0.416 - 5.88}{5.88} \times 100 = -85\%$$

$$3) \frac{0.462 - 8.53}{8.53} \times 100 = -98\%$$

Energy Consumption using Energy Meter.

Scale

\times amper 2 cm = 0.5 unit

\times amper 2 cm = 10 unit

1 division \rightarrow

100

90

80

70

60

50

40

30

20

10

0

10

0.5

10

15

20

25

30

35

40

x

Load current \rightarrow

3

2

1

0

-1

-2

-3

-200

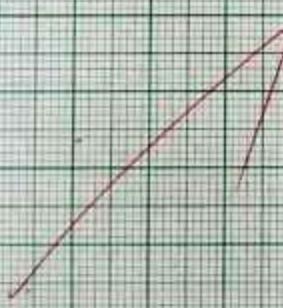

Load test on DC Shunt motor.




Aim: To conduct the brake load test on DC shunt motor and determine its performance characteristics.

APPARATUS REQUIRED:

S.No	Apparatus	Range	Type	Quantity
1	Ammeter	(0-20)A	Digital	1
2.	Voltmeter	(0-300)V	Digital	1
3.	Rheostat	370/1.7A	Wire wound	1
4	RPM meter	(0-9999) rpm	Digital	1
5	Connecting wires	-	-	As Required.

PROCEDURE:

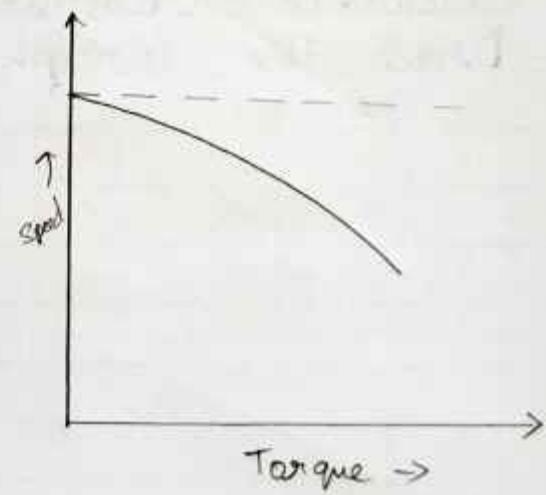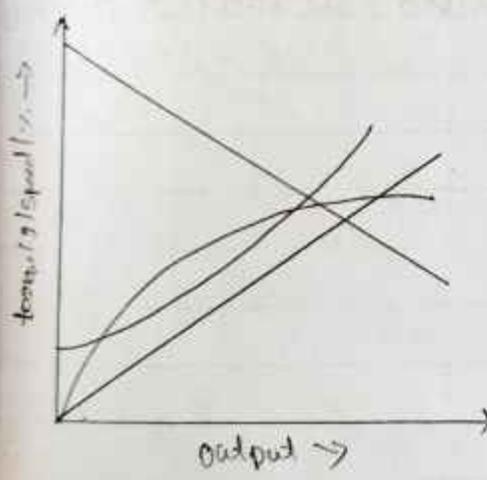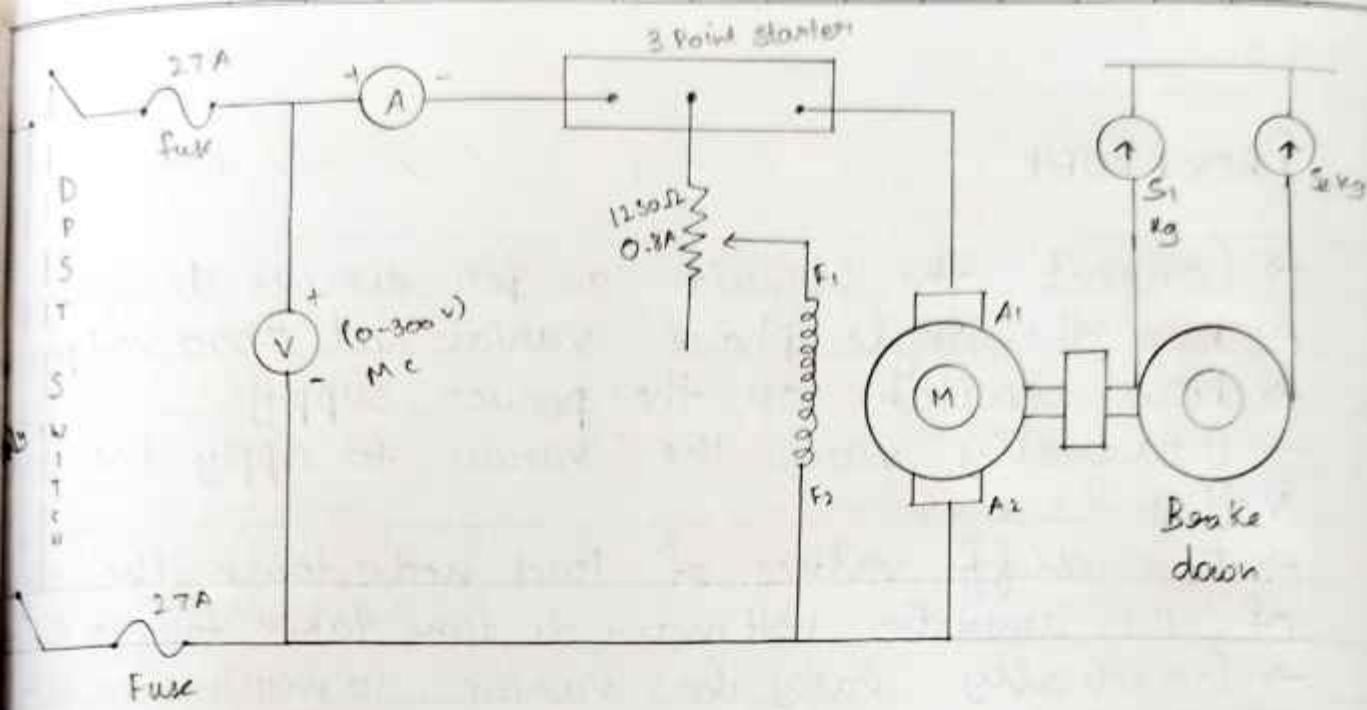- Make the connections as shown in the circuit
- Keeping the field rheostat at the minimum positions, switch on the supply and start the motor
- Adjust the speed of the motor on no load to its rated value by means of the field.
- Put the load by tightening the screws of the spring balances




	Voltage (v)	Current (A)	Speed (RPM)	Spring balance S1 S2 S3	$F(S_1-S_2) \times r \times e$	Torque (NM)	Output watt	Input watt	Efficiency (%)
	225	1.6	1486	0 0 0	0	0	0	0	0
	223	2	1480	1 0.5 0.5	4.905	0.588	91.0	446	20.40
	221	3	1466	2 1 1	9.81	1.177	272.51	663	41.10
	220	4	1464	3 1.5 1.5	14.711	1.765	273.22	880	51.04
	218	5	1460	4 2 2	19.62	2.354	360.95	1090	63.11
	216	6	1458	5 2.5 2.5	24.52	2.942	449.57	1296	64.68

De Ghent Motor

Scale


x axis 1cm = 0.5m/s

y axis 1cm = 10Nm/s

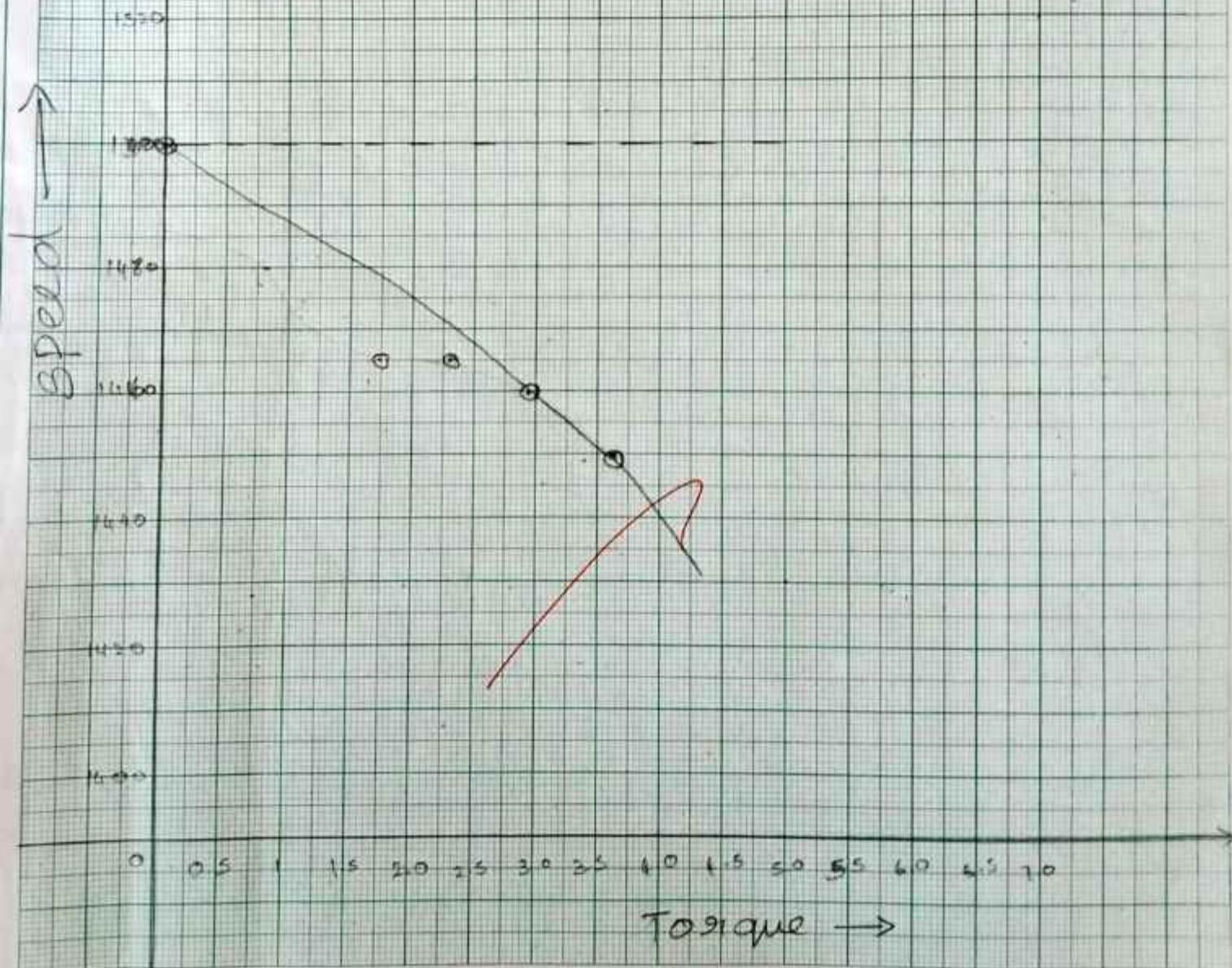

Berechnung

mit Annahmen, Ergebnis?

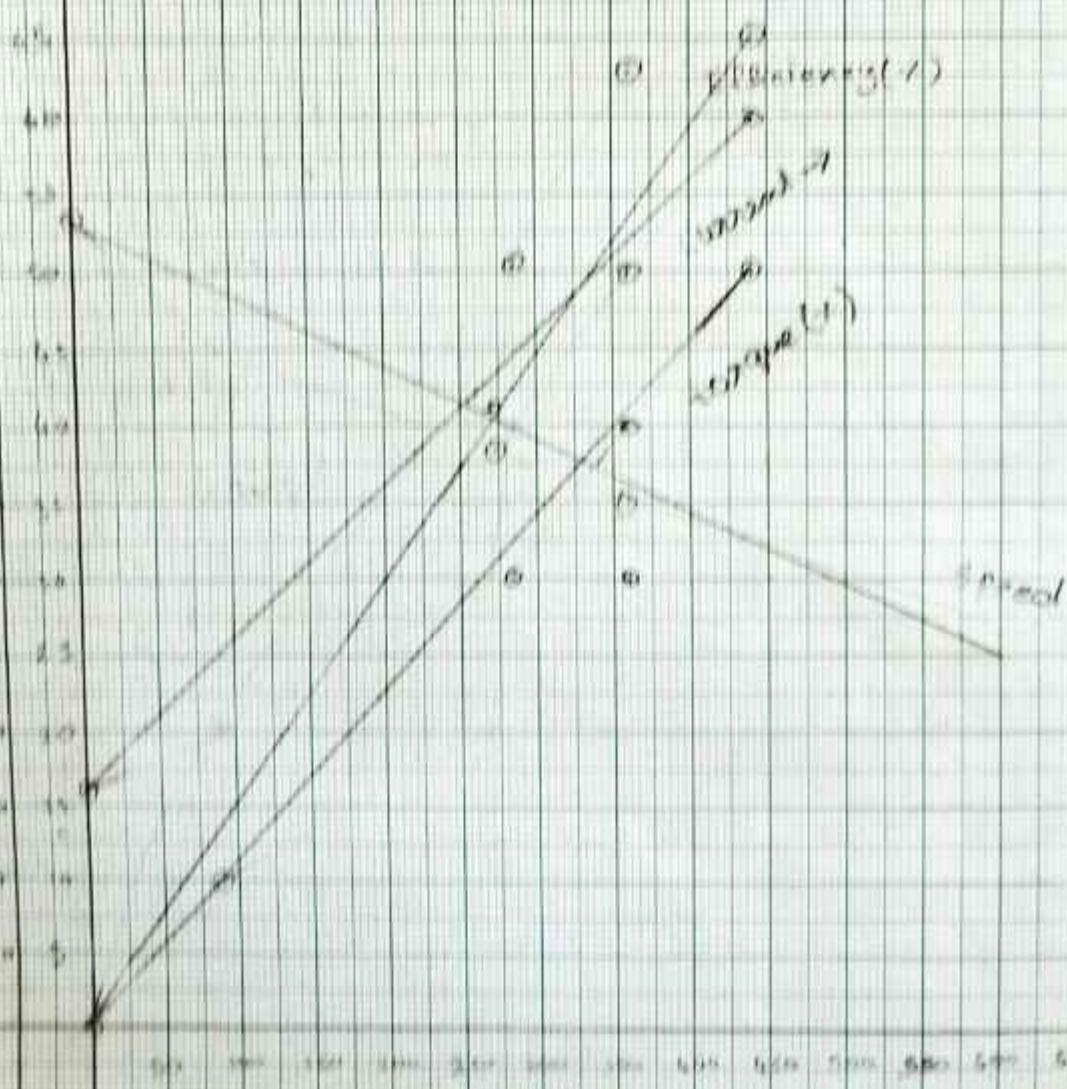

10

~~RESULT: Thus, the performance characteristics of dc shunt motor was obtained by connecting brake test.~~

Calculation:

$$F = (S_1 - S_2) \times 9.81$$

- 1) $0 \times 9.81 = 0$
- 2) $0.5 \times 9.81 = 4.905$
- 3) $1 \times 9.81 = 9.81$
- 4) $1.5 \times 9.81 = 14.71$
- 5) $2 \times 9.81 = 19.62$
- 6) $2.5 \times 9.81 = 24.52$

$$\text{Torque} = 9.81 \times (S_1 - S_2) \times R$$

- 1) $9.81 \times 0 \times 0.12 = 0$
- 2) $9.81 \times 0.5 \times 0.12 = 0.588$
- 3) $9.81 \times 1.0 \times 0.12 = 1.177$
- 4) $9.81 \times 1.5 \times 0.12 = 1.765$
- 5) $9.81 \times 2.0 \times 0.12 = 2.354$
- 6) $9.81 \times 2.5 \times 0.12 = 2.942$

$$\text{Output power} = \frac{\frac{2\pi NT}{60}}{}$$

- 1) $2 \times 3.14 \times 1471 \times 0/60 = 0$
- 2) $2 \times 3.14 \times 1471 \times 0.588/60 = 91.0$
- 3) $2 \times 3.14 \times 1471 \times 1.177/60 = 272.51$
- 4) $2 \times 3.14 \times 1471 \times 1.765/60 = 273.22$
- 5) $2 \times 3.14 \times 1471 \times 2.354/60 = 360.95$
- 6) $2 \times 3.14 \times 1471 \times 2.942/60 = 449.57$

$$\text{Input power } V \cdot I$$

- 1) ~~220~~ $\times 1.6 = 0$
- 2) $223 \times 2 = 446$
- 3) $221 \times 3 = 663$
- 4) $220 \times 4 = 880$
- 5) $218 \times 5 = 1090$
- 6) $216 \times 6 = 1296$

$$\text{Efficiency } n = \frac{\text{Output}}{\text{Input}}$$

- 1) 0
- 2) $\frac{91.0}{446} = 20.40$
- 3) $\frac{272.51}{663} = 41.10$
- 4) $\frac{273.22}{880} = 31.04$
- 5) $\frac{360.95}{1090} = 33.11$
- 6) $\frac{449.57}{1296} = 34.68$

Find stability of a System using Routh Hurwitz Criterion.

AIM:

To determine the stability of the closed loop system using Routh Hurwitz criterion for the given polynomial characteristics

$$\text{i) } s = s^4 + 2s^3 + 3s^2 + 4s + 5$$

$$\text{ii) } (s) = s^5 + 7s^4 + 6s^3 + 4s^2 + 8s + 56.$$

Tools USED:

→ Scilab Software, PC

PROCEDURE:

- Start the SCILAB software
- Open Scinotes. Type the program
- Save the file in current directory
- Compile and run the program.
- Check the console window
- Stop the program.

PROGRAM:

```

clear;
clc;
xobj(winsid(1));
mode(0);

```

$s = \gamma, s;$

$$H = s^4 + 2s^3 + 3 * s^2 + 4s + 5$$

disp(H, "The given :")

$$56 + 8s + 42s^2 + 6s^3 + 7s^4 + s^5$$

"The given characteristics equation $1 - G(s)H(s) = 0$ "

1.	6.	8.
7.	42.	56.
28.	84.	0.
21.	56.	0.
9.3333333	0.	0.
56.	0.	0.

"Rouths table ="

From Rouths table, it is clear that the system is stable.
--> |

$$5 + 4s + 3s^2 + 2s^3 + s^4$$

"The given characteristics equation $1 - G(s)H(s) = 0$ "

1.	3.	5.
2.	4.	0.
1.	5.	0.
-6.	0.	0.
5.	0.	0.

"Rouths table ="

From Rouths table, it is clear that the system is unstable.
-->

```

c = Coeff(H);
len = length(c);
r = routh_t(H);
disp(r, "Routh tables");
x = 0;
for i = 1:len
if (r(i, 1) < 0);
    x = x + 1;
end;
end;
if (x >= 1)
printf("From Routh's table, stable");
else
printf("unstable");

```

(P)
To S.H.K

RESULT:

Thus, The Stability of a system using routh's herwitz criterion is verified successfully.

Calculation:

$$S^4 + 2S^3 + 3S^2 + 4S + 3$$

S^4	1	3	5
S^3	2	4	0
S^2	1	5	0
S^1	-6	0	0
S^0	5	0	0

$$S^3 : \begin{vmatrix} 1 & 3 \\ 2 & 4 \end{vmatrix} = \frac{6-4}{2} = 1$$

$$S^2 : \begin{vmatrix} 1 & 5 \\ 2 & 0 \end{vmatrix} = \frac{10-0}{2} = 5$$

$$S^1 : \begin{vmatrix} 2 & 4 \\ 1 & 5 \end{vmatrix} = \frac{4-10}{1} = -6$$

$$S^0 : \begin{vmatrix} 1 & 5 \\ -6 & 0 \end{vmatrix} = \frac{0+30}{6} = 5$$

The System is unstable
(two sign changes)

$$S^4 + 7S^3 + 6S^2 + 42S^2 + 8S + 56$$

S^4	1	6	8
S^3	7	42	56
S^2	0	0	0
S^1	28	84	0
S^0	21	56	0

$$7S^4 + 42S^3 + 56 = 28S^3 + 84S^2$$

$$S^2 : \begin{vmatrix} 7 & 42 \\ 28 & 84 \end{vmatrix} = \frac{1176 - 585}{28} = 21$$

$$S^0 : \begin{vmatrix} 40 & 56 \\ 28 & 0 \end{vmatrix} = \frac{1568 - 0}{28} = 56$$

$$S^1 : \begin{vmatrix} 28 & 84 \\ 21 & 56 \end{vmatrix} = \frac{1764 - 1568}{21} = 9.33$$

$$S^0 : \begin{vmatrix} 21 & 56 \\ 9.33 & 0 \end{vmatrix} = \frac{522.48 - 0}{9.33} = 56$$

The System is stable.

Generation of Common discrete time Signals.

AIM:

Generate & plot the unit impulse signal unit Step signal, unit Ramp Signal, exponential signal for each signal write the SCILAB CODE to generate the signal plot the signal and Label

SOFTWARE REQUIRED:

→ Scilab 6.1.0

PROCEDURE:

- Start the Scilab Program
- Open scinotes type the program & save the Program in current directory.
- Compile & run the program
- If any error occurs in the Program, correct the error & run the program.
- For the output see the console window
- Stop the program


PROGRAM:

a) Unit Step signal


```
clear;
close;
N = 5;
t1 = -5:5;
x1 = (zeros(1,N), ones(1,N));
subplot(2,4,1);
```

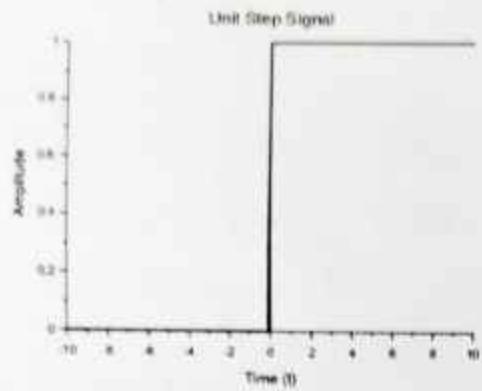b) unit impulse signal


```
clear;
close;
t1 = -5:5;
x1 = zeros(1,length(t1));
x1(1) = 1;
subplot(2,4,2);
```



Unit Impulse Signal

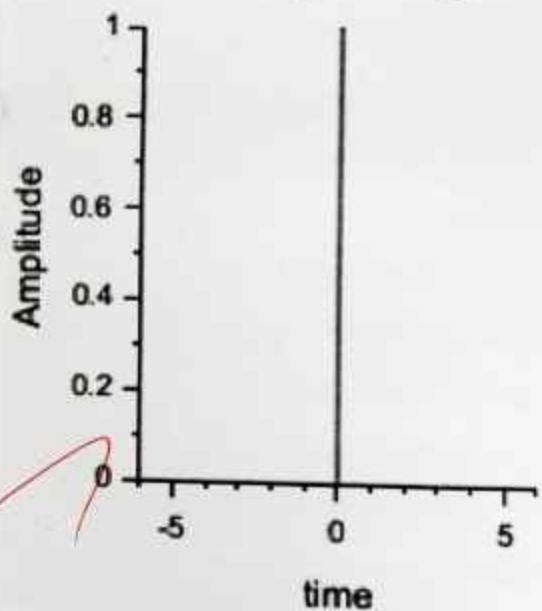

Unit Ramp Signal

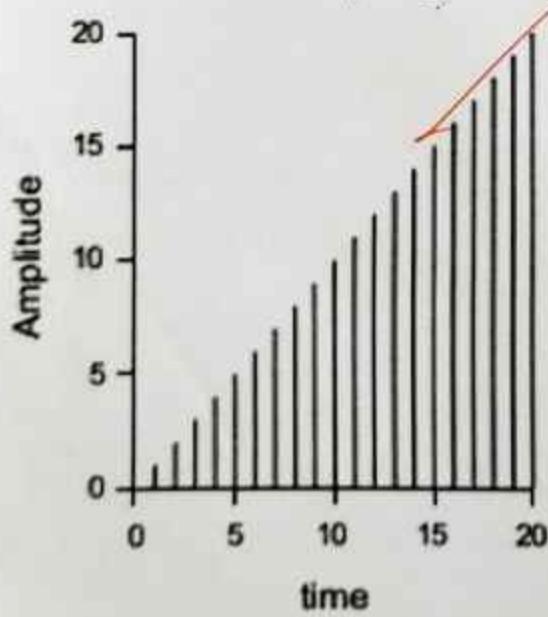

```
Plots 2d 3(t1, x2);
xlabel("time");
ylabel("Amplitude");
title("unit steps");
```

c) Unit Ramp Signal

```
clear;
close;
N = 5;
t1 = -5:5;
x1 = [zeros(1, length(t1))];
x-impulse (final(t1) = 1);
subplot (2, 4, 6);
plot 2d 3(t1, x-impulse)
xlabel ("time");
ylabel ("Amplitude");
title ("unit impulse");
```

e) Exponential Signal

```
clear;
close;
t1 = 0:10;
x-exponential = exp(-t1);
subplot (2, 4, 6);
```

```
plot 2d 3(t1, x-impulse);
```

```
xlabel("time");
ylabel("Amplitude");
title("unit impulse");
```

d) Unit ^{sineoidal} Ramp Signal

```
N = 5;
t1 = -5:5;
x1 = [zeros(1, N), 0:N];
subplot (2, 4, 6);
plot 2d 3(t1, x1);
xlabel ("time");
ylabel ("Amplitude");
title ("Ramp Signal");
```

```
plot 2d 3(t1, x-exponential);
```

```
xlabel("time");
```

```
ylabel("Amplitude");
```


```
title ("Exponential Signal");
```

a


RESULT:

Thus, the program was executed successfully.


Exponential Signal

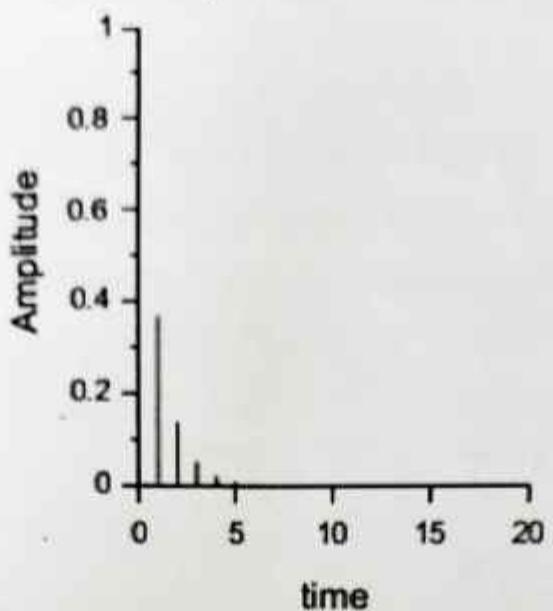

Sinusoidal Signal

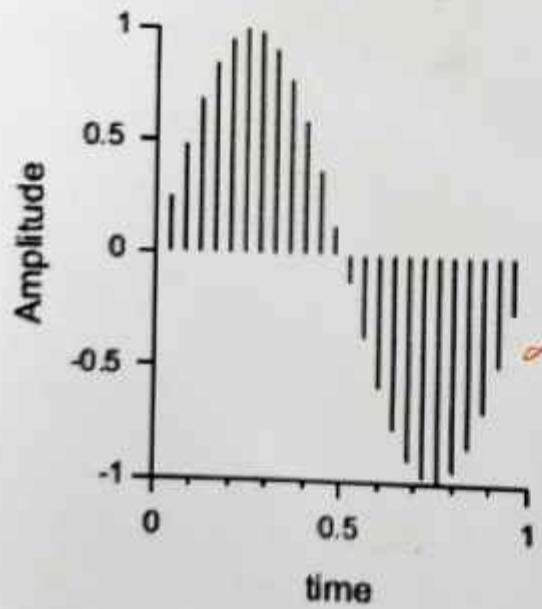

Random Signal

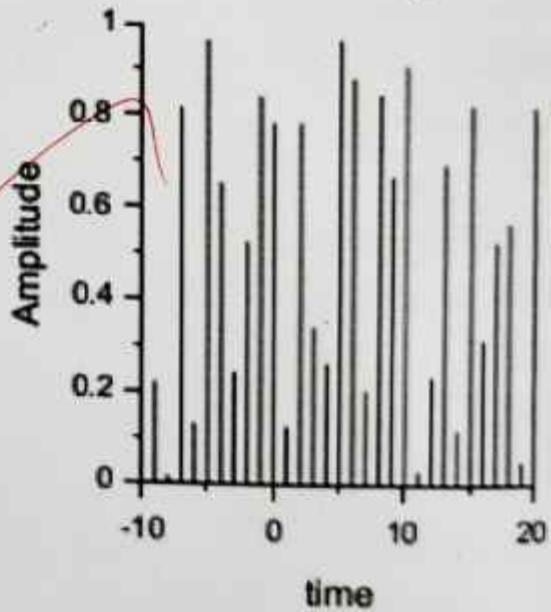

DIT - FFT & DIF - FFT Algorithm

AIM:

To compute the DFF of the given sequence

- (i) $x[n] = [1, -1, -1, -1, 1, 1, 1, -1]$ using DIT - FFT Algorithm
- (ii) $x[n] = [1, 2, 3, 4, 4, 3, 2, -1]$ using DIF - FFT Algorithm.

SOFTWARE USED:

→ Scilab 6.1.0

PROGRAM:
i) DIT - FFT Algorithm

~~clear;~~

~~close;~~

~~cls;~~

$x = [1, -1, -1, -1, 1, 1, 1, -1]$

~~// FFT computation~~

~~$x = \text{fft}(x, -1);$~~

~~$\text{disp}(x, 'x(z) = ')$~~

ii) DIF - FFT Algorithm

~~clear;~~

~~cls;~~

~~close;~~

$x = [1, 2, 3, 4, 4, 3, 2, -1]$

~~// FFT computation~~

~~$x = \text{fft}(x, -1);$~~

~~$\text{disp}(x, 'x(z) = ')$~~

~~10~~
RESULT : Thus, the program was executed successfully.

column 1 to 7
0. + 0.i -1.4142136 + 3.4142136i 0. - 2.i 1.8142136 - 0.5857864i 0. + 0.i 1.4142136 + 0.5857864i 0. + 2.i
column 8
-1.4142136 - 3.4142136i
"X(z) = "
-->

Open 2020-10-01.mws

column 1 to 7
20. + 0.i -5.828427i - 2.4142136i 0. + 0.i -0.1715729 - 0.4142136i 0. + 0.i -0.1715729 + 0.4142136i 0. + 0.i
column 8
-5.828427i + 2.4142136i
"X(z) = "
-->

Design a filter using the transformation method.

AIM:

To design a filter using the transformation

(a) Bilinear transformation

(b) Impulse invariant transformation.

SOFTWARE USED:

→ Scilab 6.1.0

PROGRAM:

(a) Bilinear transformation

clear;

clc;

close;

$s = \gamma \cdot s;$

$z = \gamma \cdot z;$

$H(s) = (s^2 + 4s + 5) / (s^2 + 0.692s + 0.504);$

$T = 1$

~~$H(z) = \text{horner}(H(s), (s(T))^*(z-1) / z + 1);$~~

~~$\text{disp}(H(z), 'H(z) = ');$~~

b) Impulse invariant transformation.

clear;

clc;

close;

$s = \gamma \cdot s;$

$T = 0.2;$

Solaris 2025 0.0 Console

```
*H(z) = *
1.4478601 +0.1783288z +1.4478601z^2
-----
0.5298913 -1.1875z +z^2
```

Solaris 2025 0.0 Console

```
*Factorized HS = "
(1): [rational]
(2): [rational]
*HZ = "
0.2014254z
-----
0.246597 -1.0381995z +z^2
```

--> |

$$HS = 101(s^1 + 2 + 7s + 10);$$

$$etts = pfss(HS);$$

disp(etts, "factorised HS = ");

$$P1 = -59$$

$$P2 = -2i$$

$$Z = 1 \cdot Z;$$

$$HZ = T^*(((-3.331(1 - e^{(P1 \times 7)} \cdot Z^{-1})) + (3.331 - 1 \times e^{(P2 \times 7)} \cdot Z^{-1})));$$

disp(HZ, "HZ = ");

(1)
(2)

RESULT.

Thus, the program was executed successfully

Design the following Butterworth filters

AIM:

To design a Butterworth filter for processing audio signals that attenuates frequencies above 0.2π or $2/\pi$ radius.

SOFTWARE USED:

→ Scilab 6.10 :

PROGRAM:

a) First Order Butterworth Low Pass Filter.

clear;

clc;

close;

s = poly(0, 's')

Omegac = 0.2 * %pi;

H = Omegac / (s + Omegac);

T = 1; // Sampling period T = 1 second.

z = poly(0, 'z');

Hz = horner(H, (2/T) + ((2-1)/(z+1))

Hw = f2mag(Hz(2), Hz(3), 512);

w = 0 : %pi / 511 : %pi;

a = gca();

a.foreground = 1;

a.front_style = 9;

x.grid(1)


xtitle('Magnitude Response of Single Pole LPF');

Disp frequency .-> Magnitude');

Scilab 2025.0.0 Console

```
"Hz (Digital Filter):"  
0.6283185 +0.6283185z  
-----  
-1.3716815 +2.6283185z
```

-->

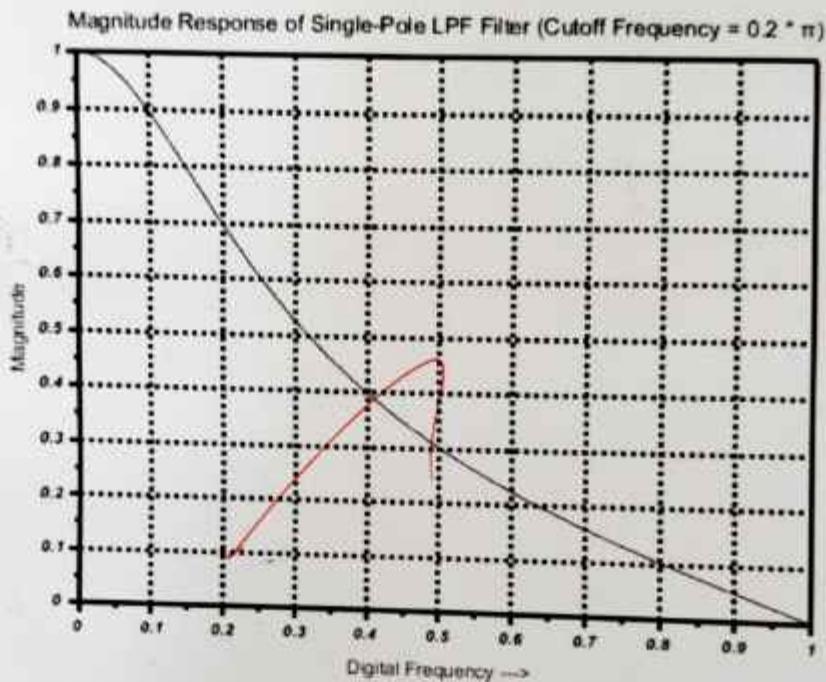

b) High Pass filter using Digital filter Transformation

clear;

clc;

close;

 $S = \text{poly}(0, 's');$ $\Omega_{\text{regac}} = 0.2 * \pi;$ $T = 1; N$ $Z = \text{poly}(0, 'z');$ $H_Z - \text{LPF} = -(\cos(\omega_c + \Omega_{\text{regac}})/2) / ((\omega_c - \Omega_{\text{regac}})/2);$ $H_W = \text{frmag}(H_Z - \text{HPF}(2), H_Z - \text{HPF}(3), (512));$ $\omega = 0.1 * \pi / 511; \gamma = \pi / 2;$ $a = \text{gac}(i);$ $a.\text{thickness} = 2;$ $a.\text{foreground} = 1;$ $a.\text{fontStyle} = 9;$

xtitle("Magnitude Response of single pole")

disp("Hz - HPF", Hz - HPF);

c) BPF HR Filter

clear;


clc;

close;

 ~~$\Omega_{\text{regac}} = p \cdot 2 * \pi / N;$~~ ~~$\Omega_{\text{regad}} = (2/s) * \pi / N;$~~ ~~$\Omega_{\text{regd}} = (3/s) * \pi / N;$~~ $Z = \text{poly}(0, 'z');$ $H_Z - \text{LPF} = (0.24s)^* (H(z_1)) / (1 - 0.509 * (z - 1))$

disp("Hz - BPF", Hz - BPF);

Magnitude Response of Single-Pole HPF Filter (Cutoff Frequency = $0.2 \cdot \pi$)

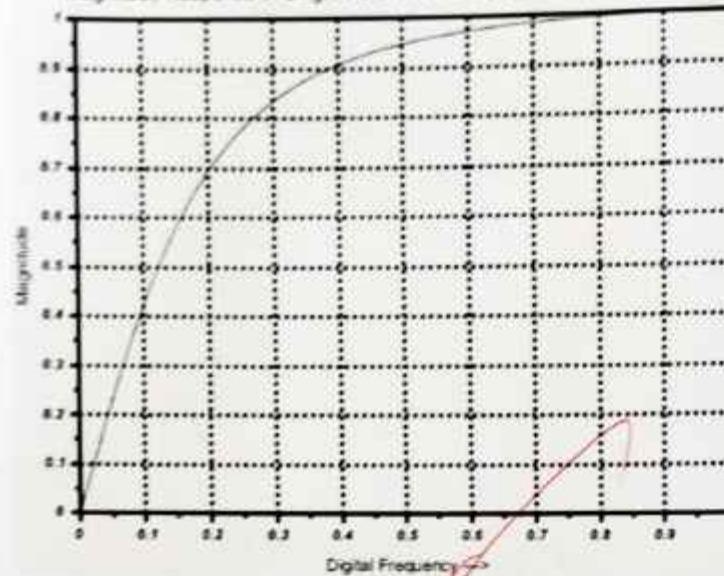


Scilab 2025.0.0 Console

```
"HZ_HPF (High-Pass Filter):"  
-0.7484757 +0.7484757z  
-----  
-0.4969514 +z
```

-->

Magnitude Response of BPF Filter

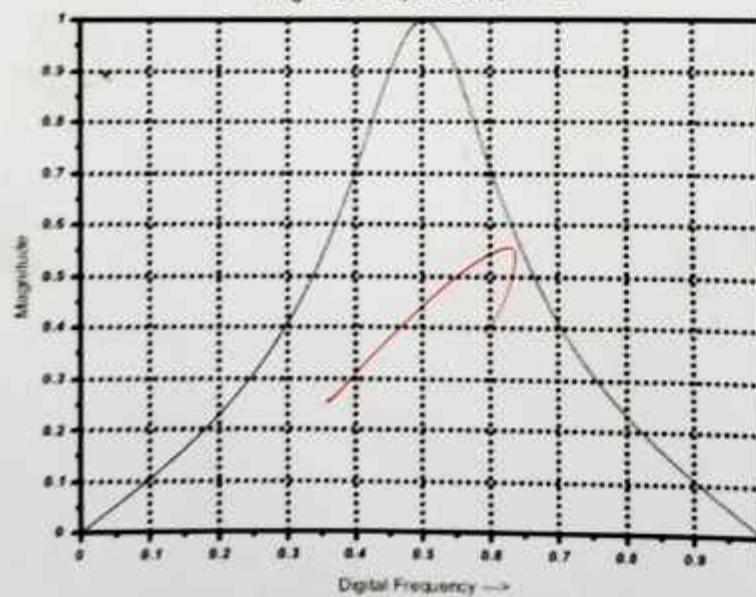

d) Band-stop filter:

clear;

clc;

close;

$$\omega_p = 0.2 \cdot \pi /$$

$$\omega_L = (2/s)^* \cdot \pi$$

$$z = \text{Poly}(0, 'z');$$

$$\text{Num} = (1/z^2) - ((2 + \alpha / Hc) * z) + ((Hk) / Hc));$$

$$H2\text{-BSF} = \text{filter}(H - \text{LPF}, \text{Num}) / \text{DEN})$$

$$H_W = \text{freqmag}(H2 - \text{BSF}(2), H_2, \text{BSF}(3), S12);$$

$$\omega = 0 : \pi / 511 : \pi /$$

$$\text{Plot}(\omega / \pi, H_W)$$

$$a = \text{gac}();$$

~~$$x = \text{grind}(1)$$~~

~~$$\text{Disp}("H2, BSF", H2 - \text{BSF});$$~~


 RESULT

Thus the program was executed successfully.

Dolph 2025 0.0 Console


"HZ_BSF"

0.7534875 -9.702D-17z +0.7534875z^2

0.5100505 -9.722D-17z +z^2

-->

Magnitude Response of BSF Filter

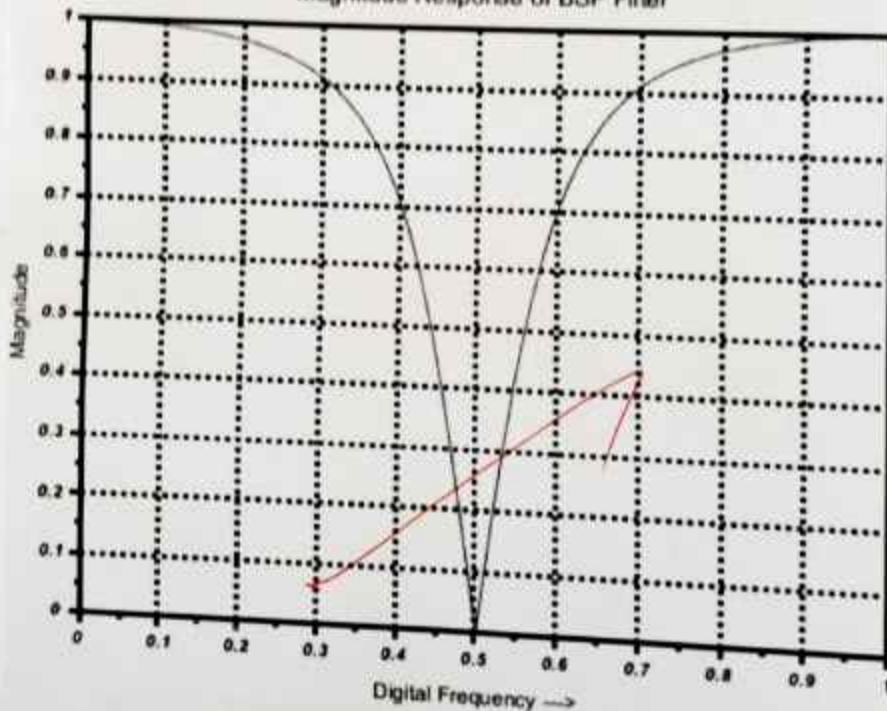

Three Phase Induction Motor

AIM:

To Study the function of three phase induction motor driver E-mobility System



APPARATUS REQUIRED:

S.No	Requirement	Quantity.
1.	750W Three Phase induction motor	1 No.
2.	Panel with DC Voltmeter, Ammeter AC meter	1 NO
3.	750W variable frequency AC Drive(vfd)	1 NO
4.	Battery Emulator /DC Drive	1 NO
5.	Human Machine Interface	1 No
6.	12 V Alternator with EV batteries	1 No .

PROCEDURE :

- Strike Ac Supply to Meter Battery Emulator/DC Drive
- Fully Rotate Potentiometer of DC control connected with Battery
- Select Forward/Reverse Mode using HMI
- Vary the Frequency using FD

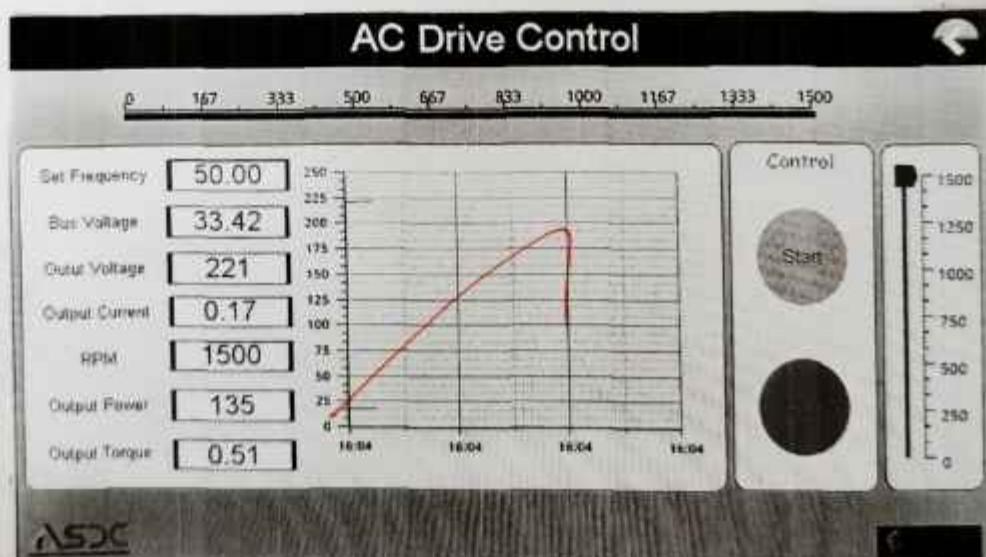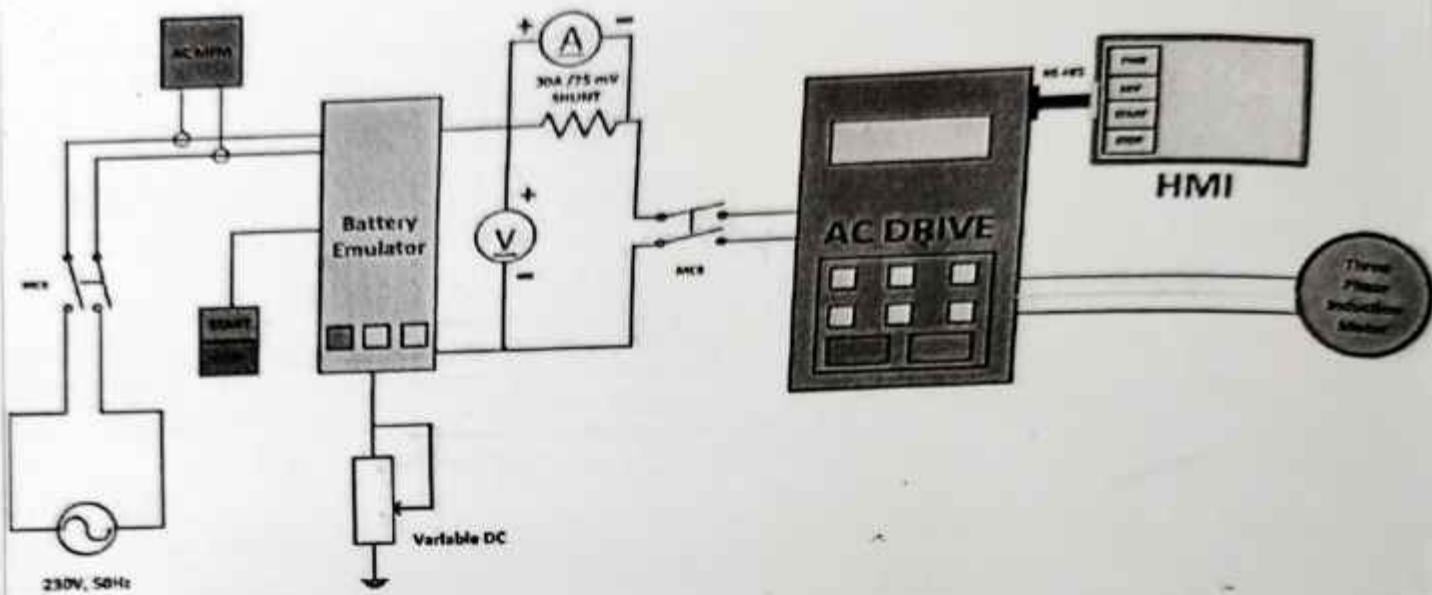Three Phase AC Induction Motor Based Model Connection Diagram



- Connect 12 V Battery in Excitation Panel
- Calculate different values given on the below Table.


~~RESULT:~~

Thus the three phase induction motor Drive System in Emobility is Performed Successfully.

AC Drive Control


0 167 333 500 667 833 1000 1167 1333 1500

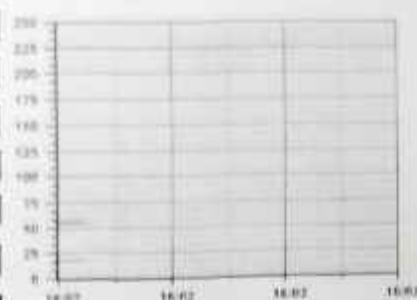Set Frequency 12.00
Bus Voltage 33.63
Output Voltage 54
Output Current 0.17
RPM 360
Output Power 54
Output Torque 0.89



Control

Start

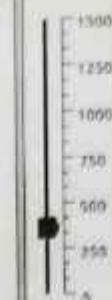

ASDC

AC Drive Control

0 167 333 500 667 833 1000 1167 1333 1500

Set Frequency 40.00
Bus Voltage 33.57
Output Voltage 177
Output Current 0.13
RPM 1200
Output Power 122
Output Torque 0.41

ASDC




Control

Start



0 167 333 500 667 833 1000 1167 1333 1500

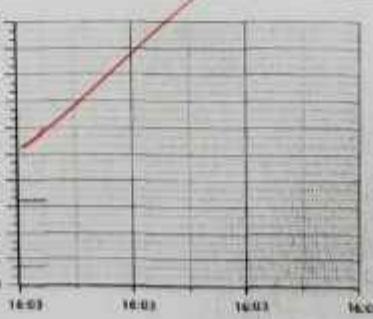Set Frequency 18.00
Bus Voltage 33.88
Output Voltage 80
Output Current 0.18
RPM 540
Output Power 81
Output Torque 0.48



Control

Start



ASDC



Verification of Ohm's Law and Kirchhoff's law

a)

AIM:

To verify Ohm's law for given resistive network.

APPARATUS REQUIRED:

S. No.	APPARATUS NAME	RANGE	QUANTITY.
1.	RPS	(0 - 30)V	1
2.	Ammeter	(0 - 200)mA	1
3.	Voltmeter	(0 - 30)V	1
4.	Resistor	1K Ω	1
5.	Rheostat	300 Ω / 2A	1
6.	Bread Board & wires	-	Required.

PROCEDURE:


- Make the connection as per circuit diagram
- Switch ON the Power supply to the RPS and apply a voltage
- Adjust the rheostat in steps & take down the readings of ammeter
- Determine and plot the slope of V-I graph.

RESULT:

Thus, the Ohm's law is verified for the given circuit.

Circuit Diagram:

HM's Law:

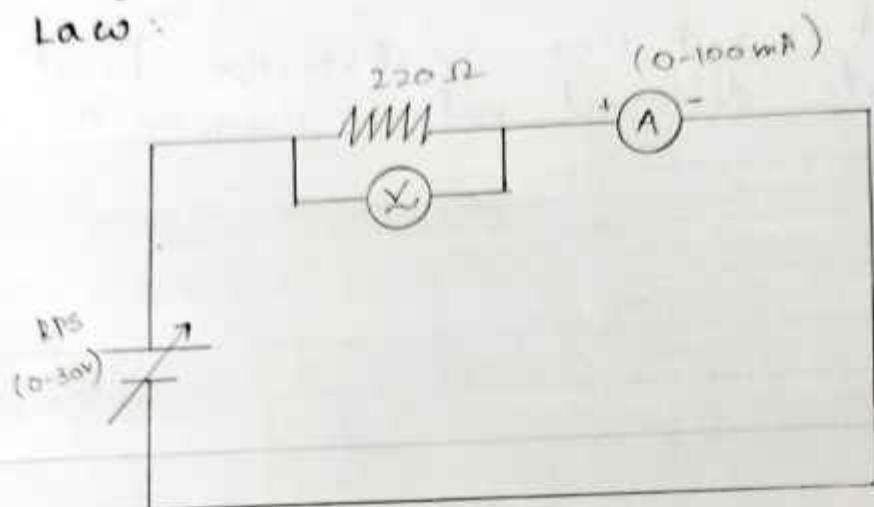

Supply	I	V	Cond _{th}	Theoretical Constant
3	2	3.5	1 kΩ	1.75
6	4	5.6	1 kΩ	1.33
8	6	7.5	1 kΩ	1.25
10	8	10	1 kΩ	1.25

Solutions


$$1) R = \frac{3.5}{2} = 1.75 \text{ k}\Omega$$

$$4) R = \frac{10}{8} = 1.25 \text{ k}\Omega$$

Model Graph

$$2) R = \frac{5.6}{4} = 1.37 \text{ k}\Omega$$
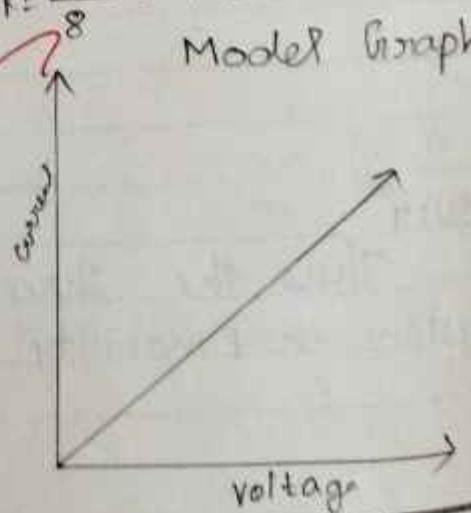
$$3) R = \frac{7.5}{6} = 1.25 \text{ k}\Omega$$



OHM'S LAW

Graph

Y-axis current = Amperes
X-axis voltage = Volts

Current →

13

12

11

10

9

8

7

6

5

4

3


2

1

0

1 2 3 4 5 6 7 8 9 10 11 12 13

Voltage →

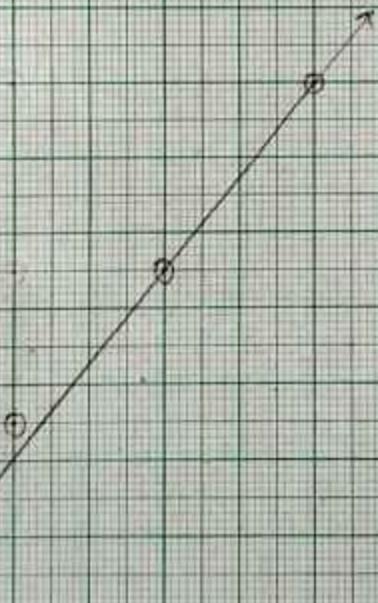

b) AIM:

To verify Kirchhoff's law for voltage and current.

APPARATUS REQUIRED:


S.NO	Name of Equipment	Type	Range	Quantity
1.	RPS	-	(0-15)V	1
2.	Bread Board	-	-	1
3.	Ammeter	Mc	(0-10), (0-5)	2
4.	Voltmeter	Mc	(0-10)(0-15)V	2
5.	Resistor	Mc	470Ω, 330Ω	1 each
6.	Connecting Wires	-	4KΩ, 4.7KΩ	As required.

PROCEDURE:

- Connections are given as per the circuit
- Apply DC Voltage to the circuit from the given RPS
- Tabulate the voltmeter and Ammeter readings for the corresponding experiment.
- Increase the voltage step by step to get different reading till the voltage reached up to 15V.
- Repeat Step 3 for different values
- Switch off the power supply after bringing RPS to the minimum voltage Position

Kirchoff's Law

KVL

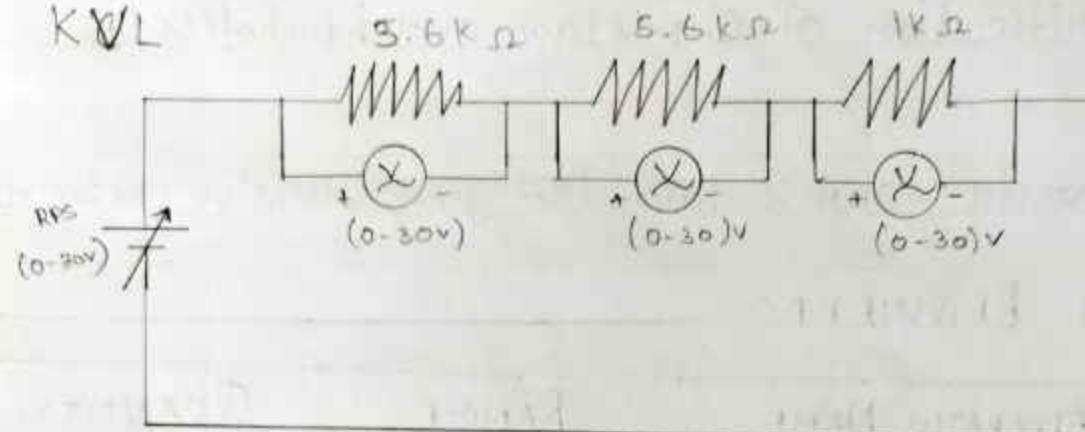

Supply vdc	Practical			Theoretical		
	V ₁	V ₂	V ₃	V ₁	V ₂	V ₃
10	4.5	4.5	1.0	4.5	4.5	0.8
20	9.1	9.0	1.7	9.1	9.1	1.6
30	13.72	13.72	2.5	13.72	13.72	2.45

Calculations:

$$R_T = 5.6 + 5.6 + 1 = 12.2$$

$$V_1 = 10$$

$$I_1 = \frac{10}{12.2} = 0.81 \text{ mA}, I_{T_2} = \frac{10}{12.2} = 1.6 \text{ mA}$$

1) $V_1 = 0.81 \times 10^3 \times 5.6 \times 10^3 = 4.536$
 $V_2 = 0.81 \times 10^3 \times 5.6 \times 10^3 = 4.53$ $V_1 + V_2 + V_3 = 9.81$
 $V_3 = 0.81 \times 10^3 \times 1 \times 10^3 = 0.81$

2) $V_1 = 2.63 \times 10^3 \times 5.6 \times 10^3 = 9.1$

$$V_2 = 1.63 \times 10^3 \times 5.6 \times 10^3 = 9.1$$

$$V_1 + V_2 + V_3 = 19.2$$

$$V_3 = 1.63 \times 10^3 \times 1 \times 10^3 = 1.6$$

3) $V_1 = 2.45 \times 10^3 \times 5.6 \times 10^3 = 13.72$

$$V_2 = 2.45 \times 10^3 \times 5.6 \times 10^3 = 13.72$$

$$V_1 + V_2 + V_3 = 29.89$$

$$V_3 = 2.45 \times 10^3 \times 1 \times 10^3 = 2.45$$

10


10

87/12

RESULT:

Thus ~~the~~ the two Kirchoff's laws was verified successfully.

KCL Circuit

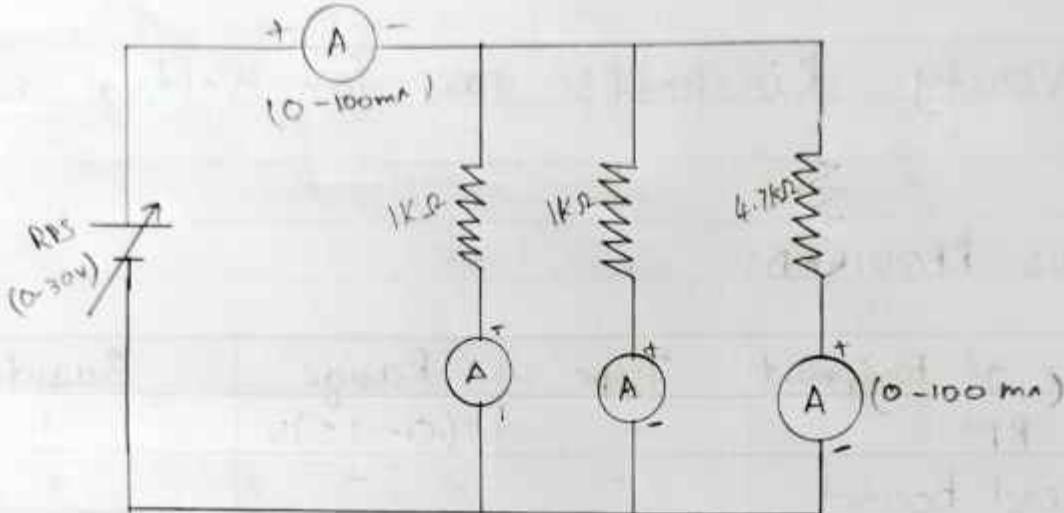

Supply	Practical			Theoretical			
	I	I ₁	I ₂	I ₃	I ₁	I ₂	I ₃
2.7	6	2.70	2.72	0.58	2.7	2.7	0.57
3.7	8	3.61	3.63	0.76	3.7	3.7	0.78
5.5	12	5.42	5.46	1.12	5.5	5.5	1.1
7.3	16	7.23	7.28	1.49	7.4	7.4	1.5

Calculations:

$$I = V/R$$

$$1) I_1 = \frac{2.7}{1} = 2.70, I_2 = \frac{2.7}{1} = 2.7, I_3 = \frac{2.7}{4.7} = 0.57$$

~~$$2) I_1 = \frac{3.7}{1} = 3.7, I_2 = \frac{3.7}{1} = 3.7, I_3 = \frac{3.7}{4.7} = 0.78$$~~

~~$$3) I_1 = \frac{5.5}{1} = 5.5, I_2 = \frac{5.5}{1} = 5.5, I_3 = \frac{5.5}{4.7} = 1.1$$~~

~~$$4) I_1 = \frac{7.3}{1} = 7.3, I_2 = \frac{7.3}{1} = 7.3, I_3 = \frac{7.3}{4.7} = 1.5$$~~

Verification of current and Voltage division Rules.

AIM:

To calculate the individual branch current and total current drawn from the power supply using current & voltage division rules.

APPARATUS REQUIRED:

S.No	Apparatus Name	Range	Quantity
1.	DC regulated Power Supply	(0-30)V	1
2.	Ammeter	(0-200)mA	4
3.	Resistor	1 k Ω , 220 Ω	Each 2
4.	Bread Board	-	- 1
5.	Connecting wires	-	Required.

PROCEDURE:


- Bring the connections as per circuit diagram
- Set the particular value in RPS
- Note down the corresponding ammeter reading
- Repeat the same for different voltages.

RESULT:

Thus the individual branch currents and total current drawn from the power supply are calculated using current and voltage division rules.


Circuit Diagram

Current Division

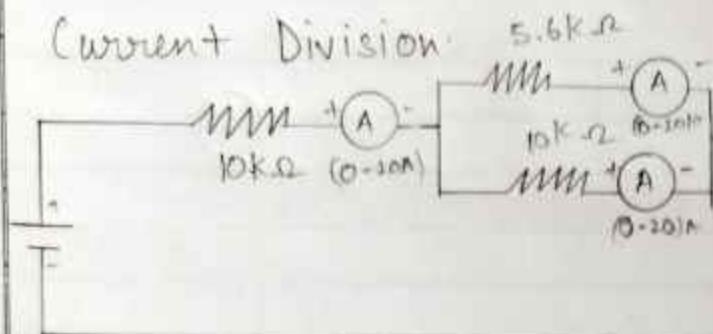

V	I ₁	I ₂	I ₃
10	0.74	0.48	0.26
15	1.11	0.72	0.39
20	1.47	0.95	0.53

Voltage division:

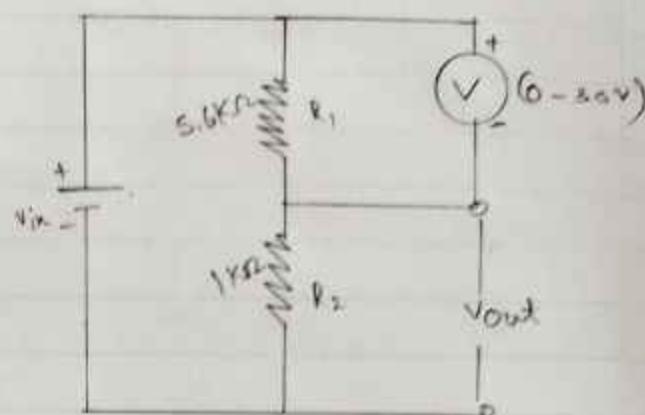

V _{in}	V ₁	V ₂
5	4.22	0.74
10	8.47	1.51
15	12.66	2.27

Calculation:

$$1) I_1 = I_2 + I_3$$

$$0.48 + 0.26 = 0.74$$

$$2) 0.72 + 0.39 = 1.11$$

$$3) 0.95 + 0.53 = 1.48$$

Calculation:

$$1) V = V_1 + V_2 = 4.22 + 0.74 = 4.96$$

$$2) V = 8.47 + 1.51 = 9.98$$

$$3) V = 12.66 + 2.27 = 14.93$$

Verification of Star delta transformation using Resistance Reduction Technique.

AIM:

To Calculate the equivalent circuit resistance using the star delta transformation technique

APPARATUS REQUIRED:

S.No	Apparatus	Range	Quantity.
1.	Resistor	2 20 Ω	2
2.	Breadboard	-	'1'
3.	Connecting wires	-	Required


PROCEDURE :

- Give the connections as per the circuit diagram
- Determine the equivalent resistance of the circuit.
- Verify the same by connecting Multimeters across PQ.

RESULT:

~~∴~~ Thus the equivalent circuit resistance is obtained using star delta transformation technique

Circuit Diagram

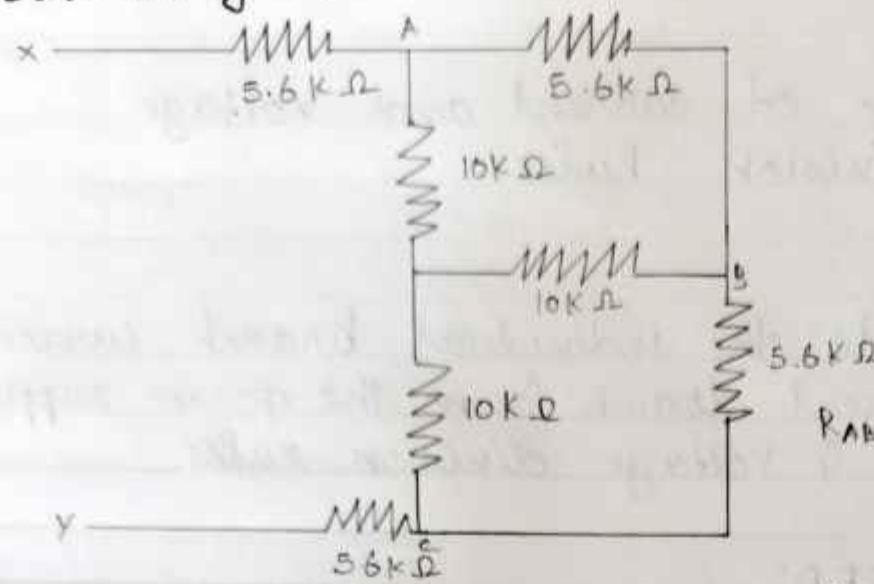

$$R_{AB} = \frac{R_{AB} + R_{BA} + R_{CA}}{R_C}$$

$$= 30\text{ k}\Omega$$

$$R_{BC} = \frac{100 + 100 + 100}{10} = 30\text{ k}\Omega$$


$$R_{AA} = \frac{100 + 100 + 100}{10} = 30\text{ k}\Omega$$

$$\Rightarrow \frac{5.6 \times 30}{35.6} = \frac{168}{35.6} = 4.72\text{ k}\Omega$$

$$\Rightarrow \frac{30 \times 11.2}{30+11.2} = 8.1\text{ k}\Omega$$

$$\Rightarrow \frac{30 \times 12.8}{30+12.8} = 8.97\text{ k}\Omega$$
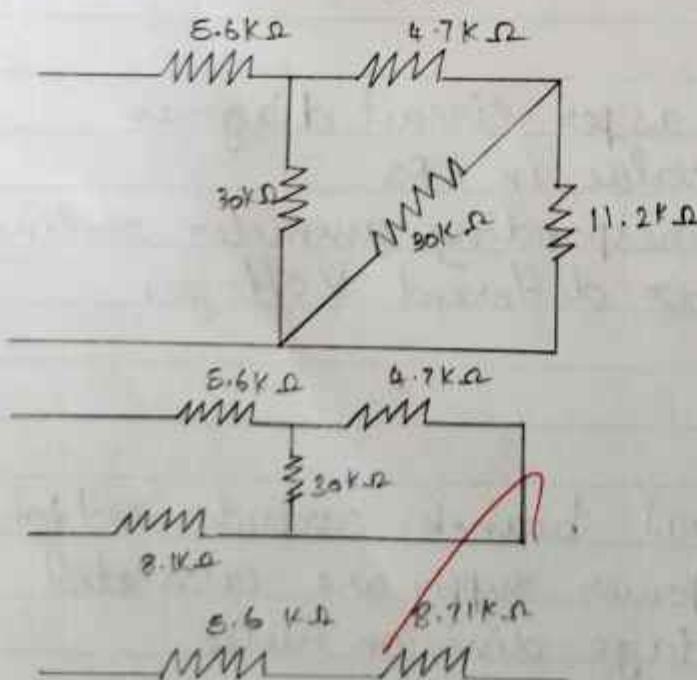
$$\Rightarrow 8.97 + 5.6 \\ = 14.5\text{ k}\Omega$$



Practical	Theoretical
$14.5\text{ k}\Omega$	$14.43\text{ k}\Omega$

Verification of Thevenin's and Norton's Theorem.

AIM:

To Verify the equivalent circuit parameters of Thevenin's Theorem and Norton's Theorem theoretically and practically.


APPARATUS REQUIRED:

S.NO	APPARATUS	RANGE	QUANTITY
1.	DC Regulated Power	(0-30)V	1
2.	Voltmeter	(0-30)V	1
3.	Ammeter	(0-200)mA	1
4.	Resistor	330 Ω , 220 Ω , 6 Ω	As required
5.	Multimeter	-	1
6.	Bread board & wires	-	As required.

PROCEDURE FOR THEVENIN'S THEOREM:


- Given the connections as per the circuit Diagram
- Measure R using the multimeter by killing sources
- Measure the V_{th} across A and B
- Measure Load current $I_L = \frac{V_{th}}{R_{th} + R_L}$
- Draw the Thevenin's Theorem.

Circuit Diagram

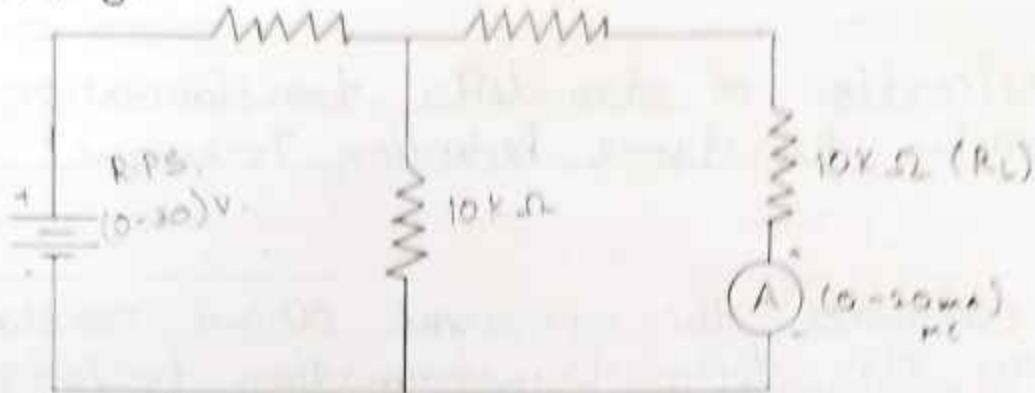


Thevenin's Theorem.

S.N.	V	I_L	I_2
1	10	0.23	0.24
2	15	0.36	0.36
3	20	0.48	0.47

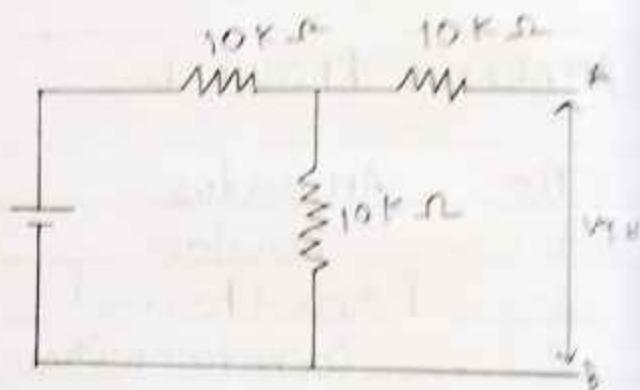

V	V_{TH}
10	4.9
15	7.4
20	9.8

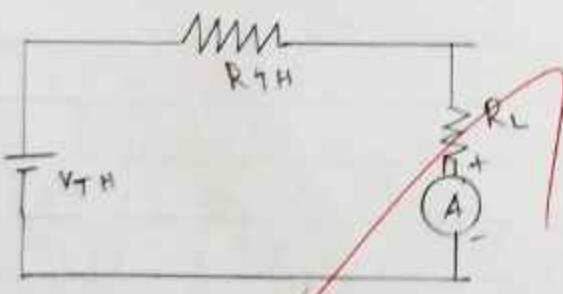

V_{TH}	I_L
4.9	0.24
7.4	0.36
9.8	0.47

$$R_{TH} \text{ Calculation: } \Delta = \begin{vmatrix} 20 & 10 \\ 20 & 20 \end{vmatrix} = 40 \Omega$$

Practical: 14.76

Theoretical: 15

$$I_2 = \frac{\Delta I_2}{\Delta} \cdot \frac{100}{40} = 0.24$$

$$\Delta I_2 = \begin{vmatrix} 20 & 20 \\ -10 & 0 \end{vmatrix} = 200$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{200}{40} = 5.0$$

$$R_{TH} = \frac{V_{TH}}{I_2} = \frac{14.76}{0.24} = 61.5 \Omega$$

$$I_L = \frac{4.9}{14.76 + 5.6} = 0.24 \text{ mA}$$

$$I_L = \frac{7.4}{14.76 + 5.6} = 0.36 \text{ mA}$$

$$I_L = \frac{9.8}{14.76 + 5.6} = 0.73 \text{ mA}$$

Calculation

Thevenin's Theorem.

$$1) I = \frac{10}{20 \times 10^3} \\ = 0.5 \times 10^{-3} A$$

$$V_{Th} = 0.5 \times 10^{-3} \times 10 \times 10^3 \\ = 5 V$$

$$2) I = \frac{15}{20 \times 10^3} = 0.75 \times 10^{-3} A \\ V_{Th} = 0.75 \times 10^{-3} \times 10 \times 10^3 \\ = 7.5 V$$

$$3) I = \frac{20}{20 \times 10^3} = 1.0 \times 10^{-3} A \\ V_{Th} = 1.0 \times 10^{-3} \times 10 \times 10^3 \\ = 10 V$$

V	V _{Th}
10	5 V
15	7.5 V
20	10 V

PROCEDURE FOR NORTON'S THEOREM:


- Give the connections as per the circuit diagram.
- Measure R_{in} using multimeter by killing sources & open circuit R.
- Measure I_N through A & B. Measure load current I_L through R.
- Draw the Norton's Equivalent's circuit.

~~Ques/Ans~~
~~RESULT~~

Thus the equivalent circuit parameter are obtained using Thvenin's & Norton's theorem.

NORTON Theorem:

Circuit Diagram:

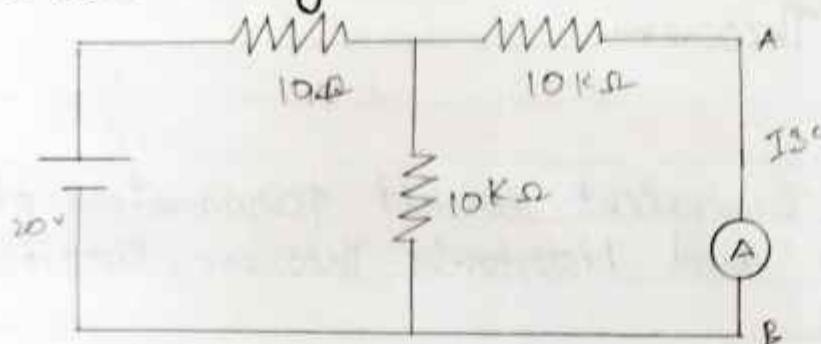

S.No	V _s	R _{th}
1	10	14.64
2	15	14.64
3	20	14.64

V	I _{SC}
10	0.3
15	0.5
20	0.6

R_{TH}:

$$I_{SC} = \frac{V_s}{R_{th}}$$


$$1) \frac{4.0}{14.64} = 0.33$$

$$2) \frac{7.4}{14.64} = 0.50$$

$$\text{Theoretical: } 15.0$$

$$3) \frac{9.8}{14.64} = 0.66$$

I _{SC}	I _L
0.3	0.22
0.5	0.36
0.6	0.43

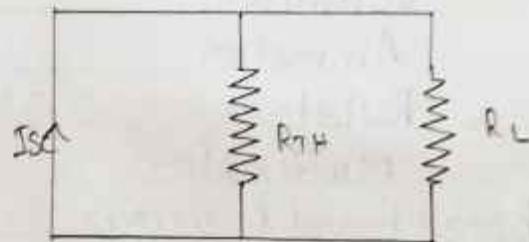

Calculation:

$$V = IR$$

$$2) \Delta I_2 = \begin{vmatrix} 20 & 20 \\ -10 & 0 \end{vmatrix} = 200$$

$$\begin{vmatrix} 10 \\ 0 \end{vmatrix} = \begin{vmatrix} I_1 \\ I_2 \end{vmatrix} \begin{vmatrix} 20 & -10 \\ -10 & 25.6 \end{vmatrix}$$

$$I_3 = \frac{200}{412} = 0.49$$

$$I_1 = 5A - 10A = 412$$

$$3) \Delta I_2 = \begin{vmatrix} 20 & 15 \\ -10 & 0 \end{vmatrix} = 0 + 150 = 150$$

$$I_2 = \frac{\Delta I_2}{\Delta}$$

$$I_2 = \frac{150}{412} = 0.36$$

$$1) \Delta I_2 = \begin{vmatrix} 20 & 0 \\ -10 & 0 \end{vmatrix} = 200$$

$$I_2 = 0.24$$

Verification of Superposition and Maximum Power transfer Theorem.

AIM: To verify Maximum Power transfer theorem

APPARATUS REQUIRED:

S.NO	APPARATUS REQUIRED	RANGE	QUANTITY
1	DC Regulated Power Supply	(0-30)V	1
2.	Voltmeter	(0-30)V	1
3.	Ammeter	(0-200)mA	1
4.	Resistor	330Ω, 220Ω	Each two
5.	Multimeter	-	1
	Bread board	-	1
	wires	-	Required

PROCEDURE:


- Give the connections as per circuit Diagram
- Measure R_m Using a multimeter.
- Measure V_m across 220Ω (R_L)
- Measure current I_1 through R_L
- Calculate the max power transformed to the load.

RESULT:

Thus the maximum Power theorem is verified.

Circuit Diagram:

Maximum Power Transfer Theorem

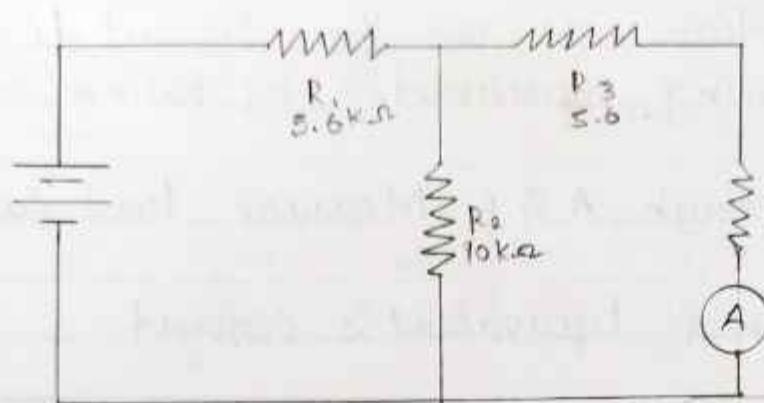

$$\frac{5.6 \times 10}{15.6} \left(\frac{R_2}{R_{12}} \right) \\ = 3.58 \\ 3.58 + 5.6 \\ = 9.18$$

No	R_L	I_L	$P = I_L^2 \times R$
1	1	1.2	1.44
2	2	1.1	2.42
3	3	1.0	3.00
4	4	0.9	0.032
5	5	0.8	0.032
6	6	0.08	0.0384
7	7	0.07	0.343
8	8	0.7	3.92
9	9	0.7	4.41
10	10	0.6	3.6

5) $0.08 \times 0.08 \times 5 = 0.032$

6) $0.08 \times 0.08 \times 6 = 0.38$

7) $0.07 \times 0.07 \times 7 = 0.34$

8) $0.7 \times 0.7 \times 8 = 3.92$

9) $0.7 \times 0.7 \times 9 = 4.41$

10) $0.6 \times 0.6 \times 10 = 3.6$

1) $1.2 \times 1.2 \times 1 = 1.44$

2) $1.1 \times 1.1 \times 2 = 2.42$

3) $1.0 \times 1.0 \times 3 = 3.00$

4) $0.09 \times 0.09 \times 4 = 0.032$

Maximum Power Transfer

Scale

X axis 1cm = 1 unit
Y axis 1cm = 0.5 units

4.5

4.0

3.5

3.0

2.5

2.0


1.5

1.0

0.5

0

1 2 3 4 5 6 7 8 9 10 11 12

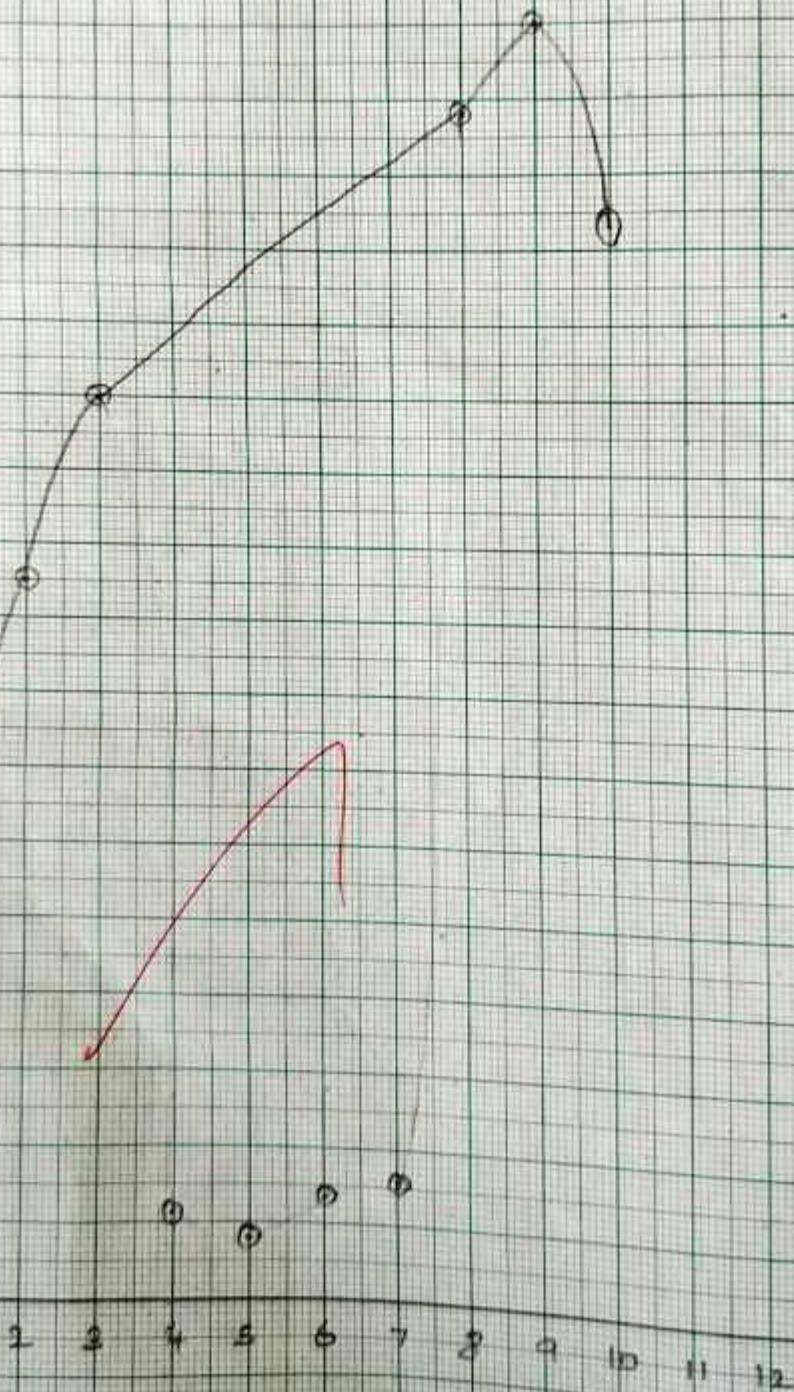

b.

AIM:

To determine the current flow through the load resistor using superposition theorem.

APPARATUS REQUIRED:

SNo	Apparatus Name	Range	Quantity
1.	DC Regulated Power Supply	(0-30)V	2
2.	Voltmeter	(0-30)V	1
3.	Ammeter	(0-200)ma	1
4.	Resistor	1K Ω , 220Ω, 330Ω	Each one
5.	Multimeter	-	1
6.	Bread Board	-	1
7.	Connecting wires	-	Required

PROCEDURE:


- Given the connections as per the circuit
- Measure current flow through 1K Ω
- Short circuit 15V source
- Measure current flow through 1K Ω
- Short circuit 20V
- Verify the net current through 1K Ω resistor.

RESULT:


Thus the Superposition theorem was verified.

Circuit Diagram:


Superposition theorem:

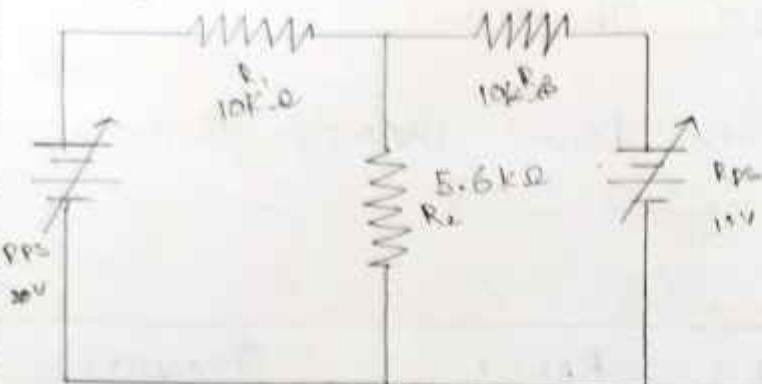

V_1	V_2	V_L
10	10	0.94
15	30	2.14
20	30	2.37

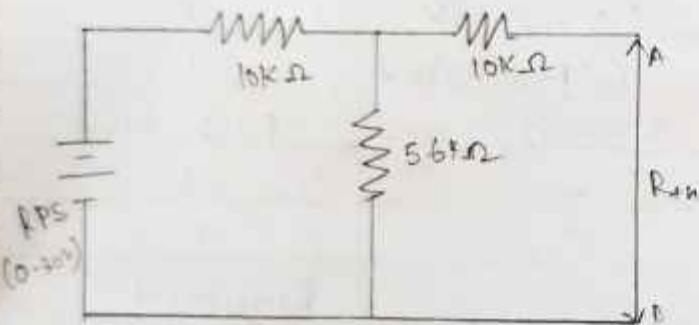

V_1	I_L
10	0.47
15	0.70
20	0.95

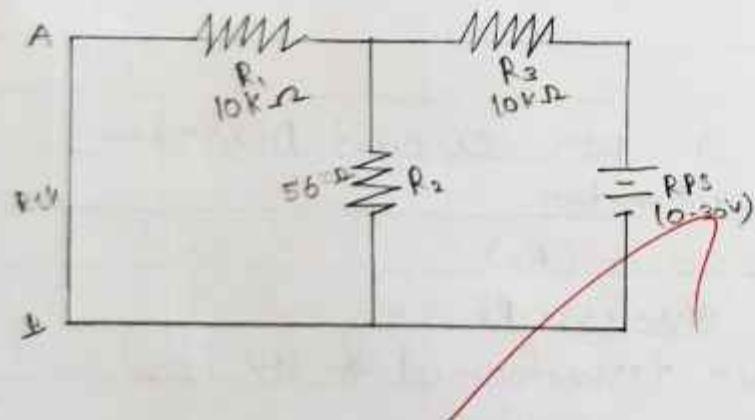

V_2	I_L
10	0.47
30	1.42
30	1.42

Calculations:

$$\begin{vmatrix} R & | & I_1 \\ & | & I_2 \end{vmatrix} = \begin{vmatrix} 15 & \\ -30 & \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 15.6 & -5.6 \\ -5.6 & 15.6 \end{vmatrix} = 212$$

$$\Delta I_{L1} = \begin{vmatrix} 15 & -5.6 \\ -30 & 15.6 \end{vmatrix} = 66$$

$$I_1 = \frac{\Delta I_{L1}}{\Delta} = \frac{66}{212} = 0.31$$

$$\Delta I_{L2} = \begin{vmatrix} 15.6 & 15 \\ -5.6 & -30 \end{vmatrix} = -234$$

$$I_2 = \frac{\Delta I_{L2}}{\Delta} = \frac{-234}{212} = -1.10$$

$$I_L = I_1 - I_2 = 0.31 + 1.10 \\ = 1.42 \text{ mA}$$

$$\Delta V_1 = \frac{V_1 - V_2}{\Delta} = 0.39$$

$$I_{L1} = 1.10 - 0.39 = 0.71$$

i) V_2 is shorted

$$\begin{vmatrix} 30 & -5.6 \\ 0 & 15.6 \end{vmatrix} = 3.12 \text{ mA}$$

$$\Delta = 212$$

$$\Delta I_{L1} = \begin{vmatrix} 15.6 & 30 \\ -5.6 & 0 \end{vmatrix}$$

$$\Delta I_{L2} = 168$$

$$I_2 = \frac{168}{212} = 0.79$$

$$I_{L2} = 2.20 - 0.79 = 1.41$$

$$I_L = I_{L1} + I_{L2}$$

$$= 0.71 + 1.41$$

$$= 2.12 \text{ mA}$$

i) V_2 is shorted:

$$\Delta = 212$$

$$I_{L1} = \begin{vmatrix} 15 & -5.6 \\ 0 & 15.6 \end{vmatrix}$$

$$= 234 - 0 = 234$$

$$I_{L1} = \frac{234}{212} = 1.10$$

$$\Delta I_{L1} = \begin{vmatrix} 15.6 & 15 \\ -5.6 & 0 \end{vmatrix}$$

$$= 84$$

Output Characteristics of LVDT

AIM:

To plot the output characteristics of LVDT

APPARATUS REQUIRED:

S.No	Apparatus	Quantity
1.	LVDT KIT	1
2	Multimeter	1
3	Connecting wires	As required.


PROCEDURE:

- Connect the circuit according to circuit Diagram
- Switch on the power supply.
- The wire is initially brought to null position.
- First turn the nut in clockwise direction to move core inwards.
- Now turn the nut in anticlockwise direction to move the core outwards.
- Plot the graph from observation.


RESULT:

Thus the output characteristics of LVDT plotted.

Circuit Diagram:

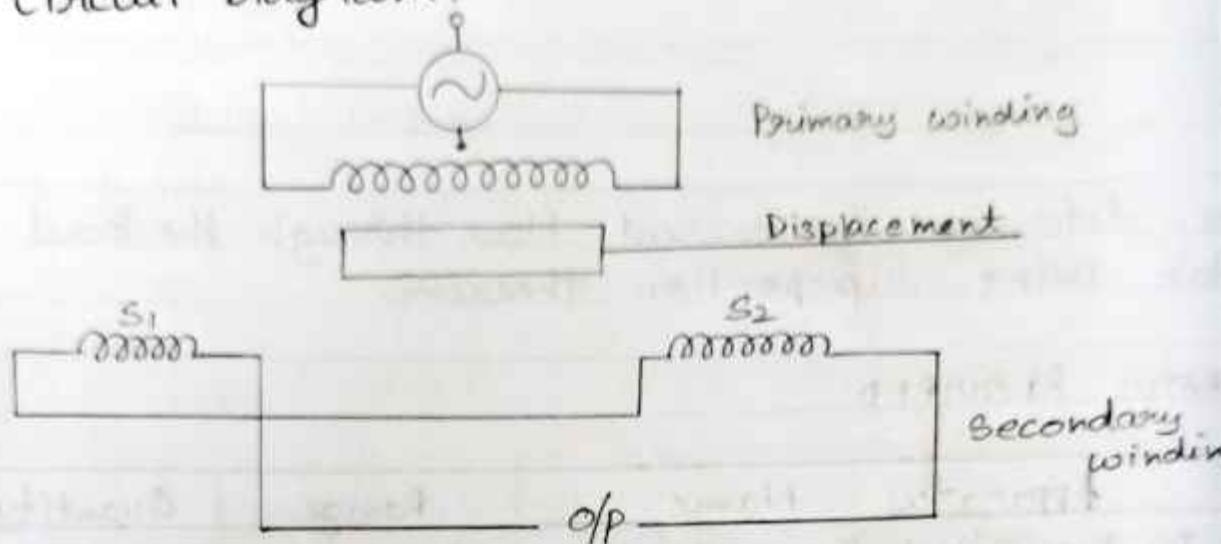


	Displacement (mm)	Voltage (v)
	3	5
	6	4
	6.5	2
	7	1
	8	0
	8.5	-0.5
	9	-1
	10	-2
	10.5	-3.5

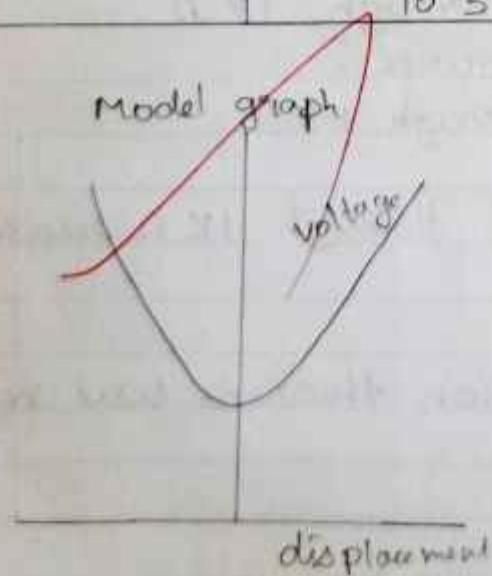

Output characteristics of LVDT

Scale
x axis cm.
y axis rev.

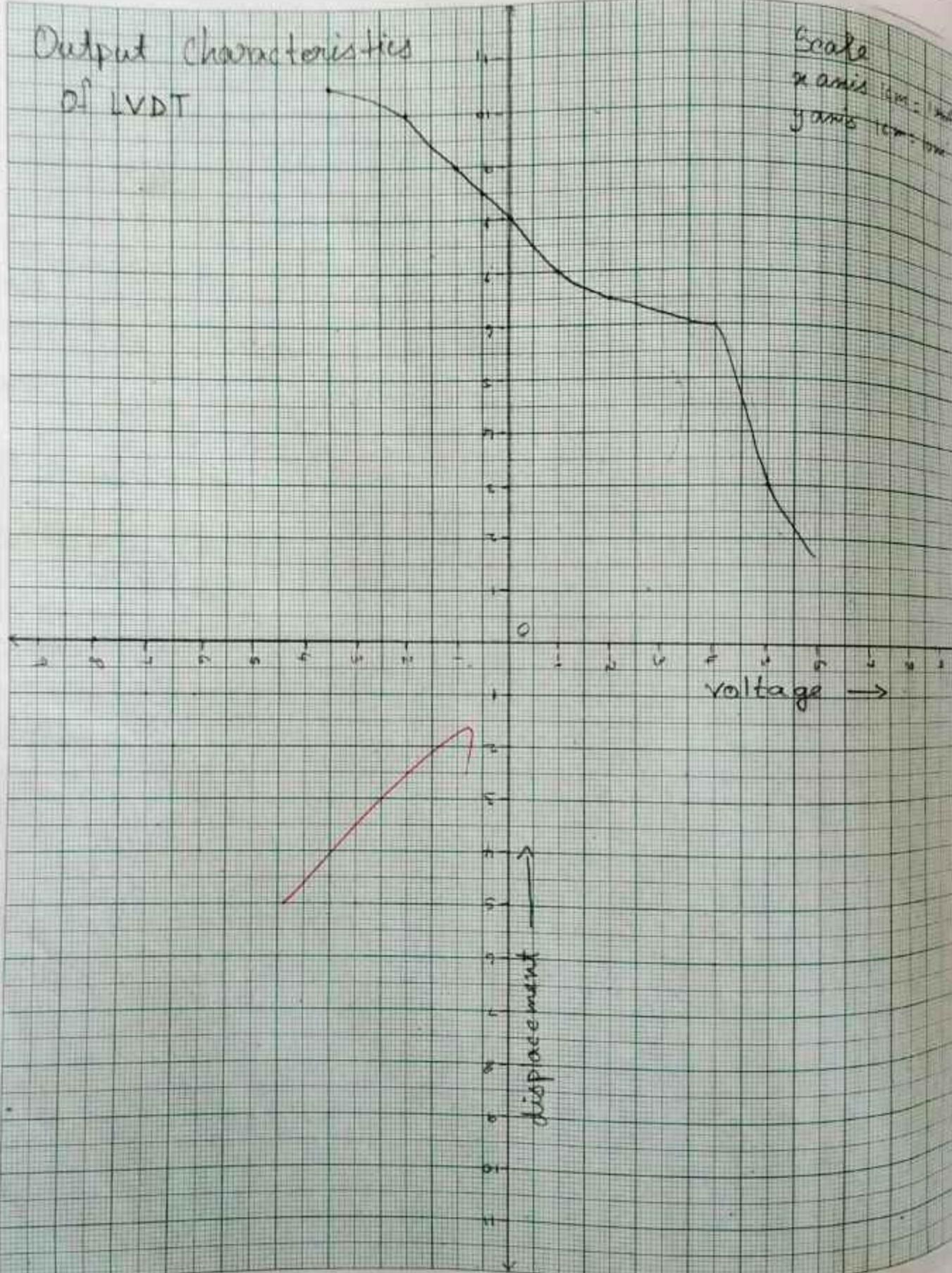

a)

Staircase Wiring

AIM:

To Control the status of given lamp using two way switches.

APPARATUS REQUIRED:

S.NO	Apparatus	Range/Type	Quantity
1	Incandescent Lamp	60W/40W	1
2	SPDT	230V	2
3	Lamp holder	Pendant type	1
4	Line Tester	500K / Papenfusio	1
5	3Pin Plug	SA/230V	1
6	wire cutter	Pye 950	1
7	wires	12A/1.3g/m o.r.t.w.	As require

PROCEDURE:


- A piece of wire is connected to phase & other end to middle point of SPDT switch.
- Another point of Lamp holder is connected to neutral
- Upper point of SPDT is connected to upper point of Switch 2
- Circuit is tested that all switch connection.

RESULT:


Thus the status of given lamp was controlled and tested under direct & indirect connection.

Circuit Diagram

Direct Connection

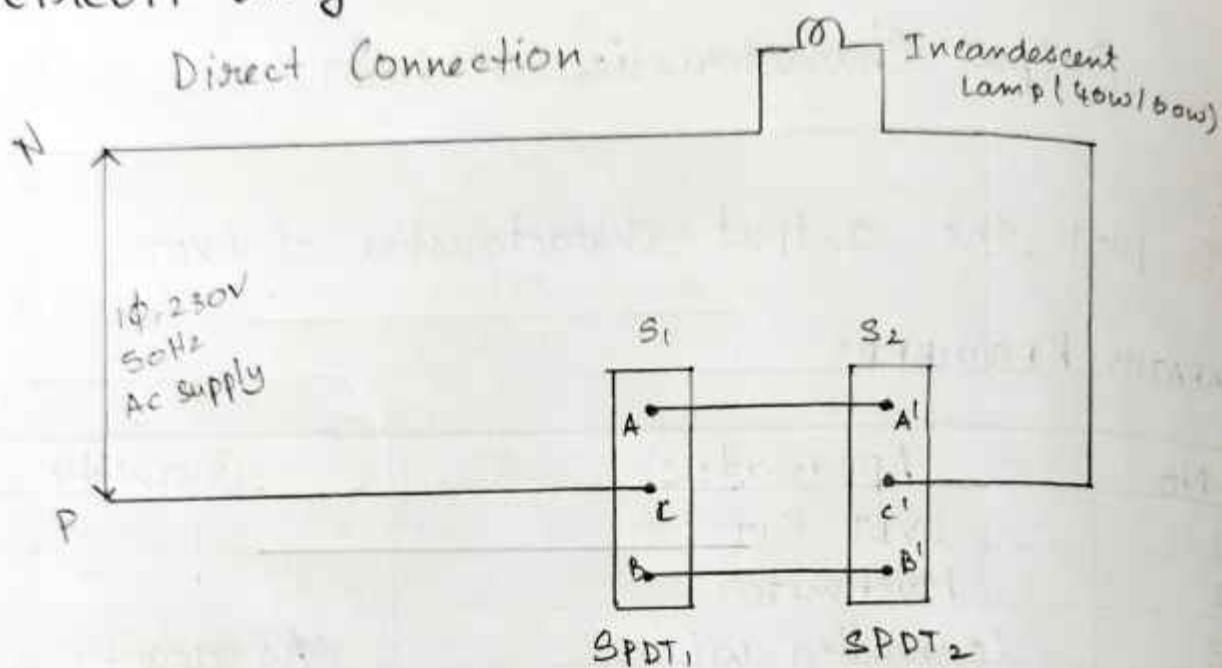

Indirect Connection

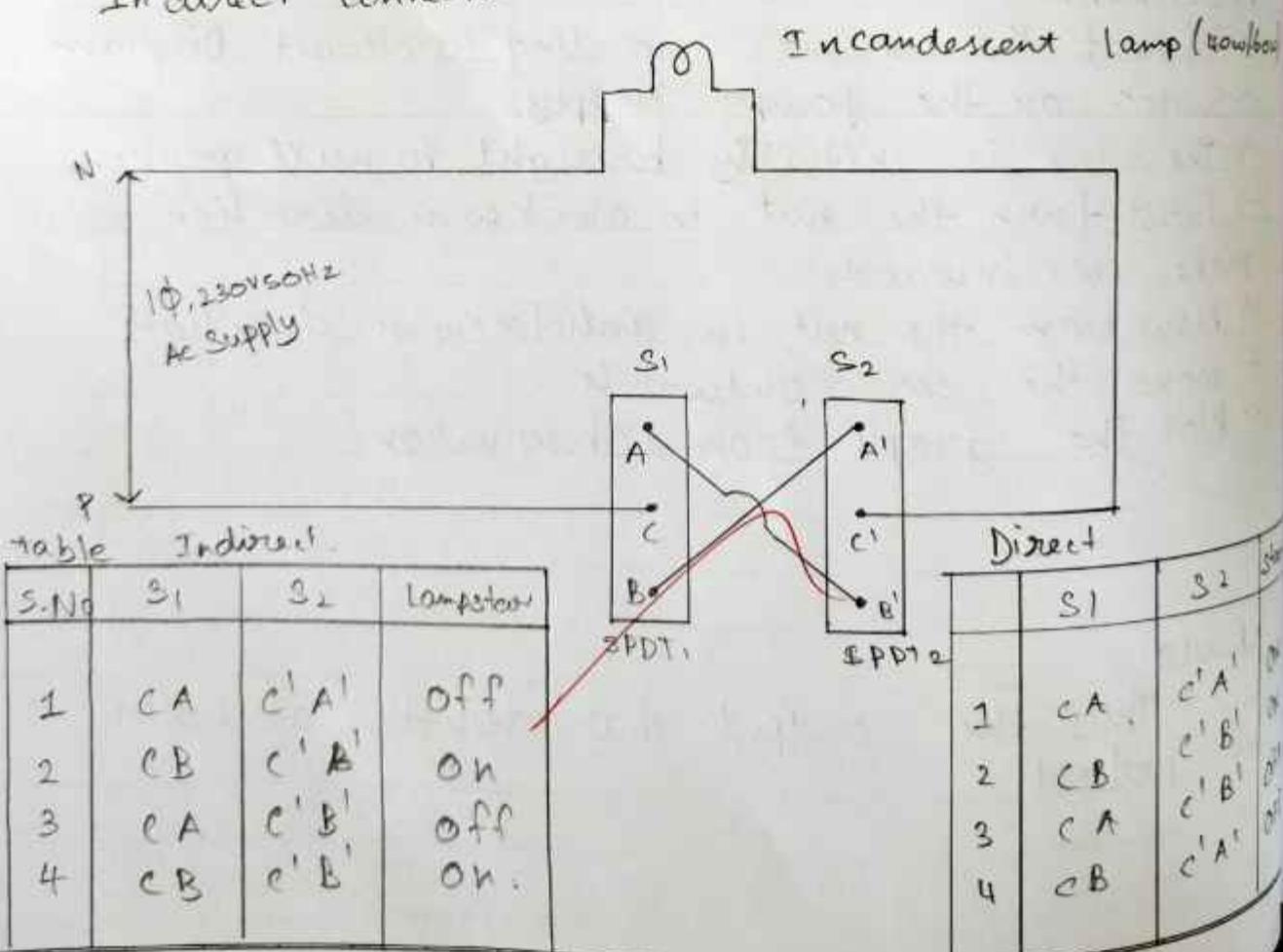

b.

Fluorescent tube wiring

AIM:

To prepare wiring for the fluorescent tube light with switch control.

APPARATUS REQUIRED:

SNo	APPARATUS	Range	Quantity.
1.	Tubelight with fitting	-	1
2.	Joint clips	-	As required
3.	Switch	-	1
4.	wires	-	As required
5.	Screws	-	As required
6.	Switch board	-	1

PROCEDURE:

- Mark the switch & tubelight location points & draw lines for wiring on the wooden board.
- Place wires along the lines & fix them with help of clips
- Complete the wiring as per the circuit
- Test the working of tube light by giving electric supply.

RESULT:

Thus the wiring for the tubelight is completed

~~It is tested.~~

Circuit Diagram:

